

①

2

Symbols and Abbreviations:

| Quantity | Symbol | unit | units |
|-----------------|----------|-------------------|------------|
| 1. Resistance | R | ohm | Ω |
| 2. Capacitance | C | farad | F, μF |
| 3. Inductance | L | henry | H |
| 4. Impedance | Z | ohm | Ω |
| 5. Resistivity | ρ | ohm meter | Ωm |
| 6. Conductivity | σ | siemens per meter | S/m |
| 7. Admittance | Y | siemens | S |
| 8. Current | I | ampère | A, mA, |
| 9. Potential | V | volt | V, mV, k |
| 10. Frequency | f | hertz | Hz, kHz, |
| 11. Power | P | Watt | W, kW, M |
| 12. Energy | W | joule, watt hour | J, Wh |
| 13. Force | F | Newton | N |
| 14. Efficiency | η | unitless | |

Abbreviations for Multiples and Submultiples

| | | |
|-------|-------|------------|
| T | tera | 10^{12} |
| G | giga | 10^9 |
| M | mega | 10^6 |
| K | kilo | 10^3 |
| d | deci | 10^{-1} |
| c | centi | 10^{-2} |
| m | milli | 10^{-3} |
| μ | micro | 10^{-6} |
| n | nano | 10^{-9} |
| p | pico | 10^{-12} |

International System of Units


The IS of U known as (SI)


The (SI) ~~has~~ has six fundamental units


| <u>Quantity</u> | <u>symbol</u> | <u>unit</u> | <u>Abbreviation</u> |
|------------------------|---------------|-------------|---------------------|
| (1) Length | L | metre | m |
| (2) mass | m | Kilogram | Kg |
| (3) time | t | second | S |
| (4) Electric current | I | ampere | A |
| (5) temperature | T | Kelvin | K |
| (6) Luminous intensity | E_m | Candela | Cd |

Electric circuit and its elements:

An elec circuit or elec. network is an a collection of electrical elements interconnected in some specified way so that a closed path is available for the current to flow. The two terminals a and b of a source of elec. energy are connected by wires to resistor, inductors, capacitors or other solid state devices.

Resistance: is the first circuit element used to represent energy dissipation as heat or radiation energy.  (circuit symbol)

Inductance: is the second circuit element used to represent the energy stored in a magnetic field and measured in henrys. 

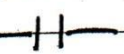Capacitance: is the third circuit element used to represent charge storage and consequently, energy stored in elec. field and is measured in Farad. 

(2)

EXP

Calculate the downing of energy in the voltage source of the following cases:



1. before the load

2. if put the load $R_L = 75\Omega$

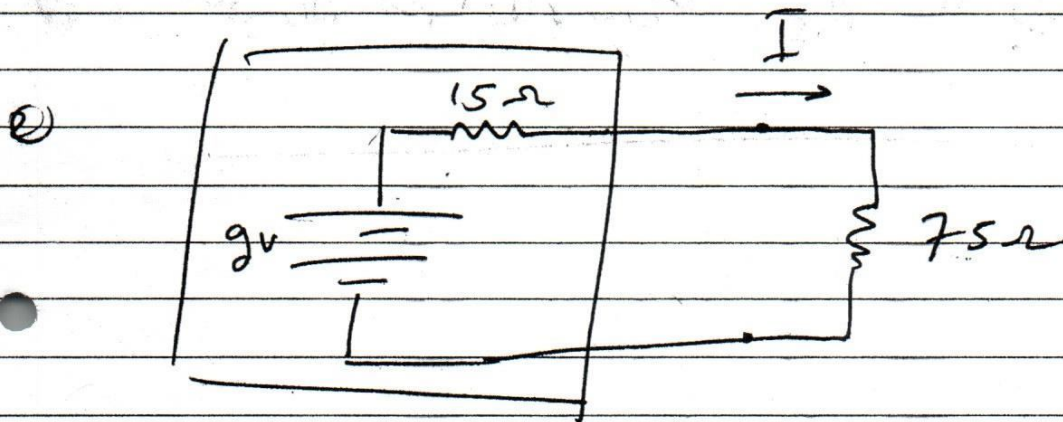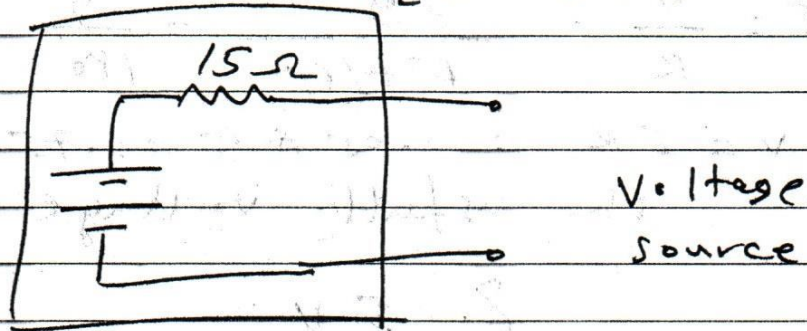3. if put the load $R_L = 165\Omega$

if the battery has $9V$ and internal resistance of 15Ω

①
if not load
that means
the current $9V$
its zero
and down of
the voltage its zero.




we can calculate the current used by
~~low~~ ohms law

$$I = \frac{V}{R} = \frac{9}{15 + 75} = \frac{9}{90} = 0.1 \text{ A}$$

The down of the voltage:

$$V = IR = 15 \times 0.1 = 1.5 \text{ V}$$

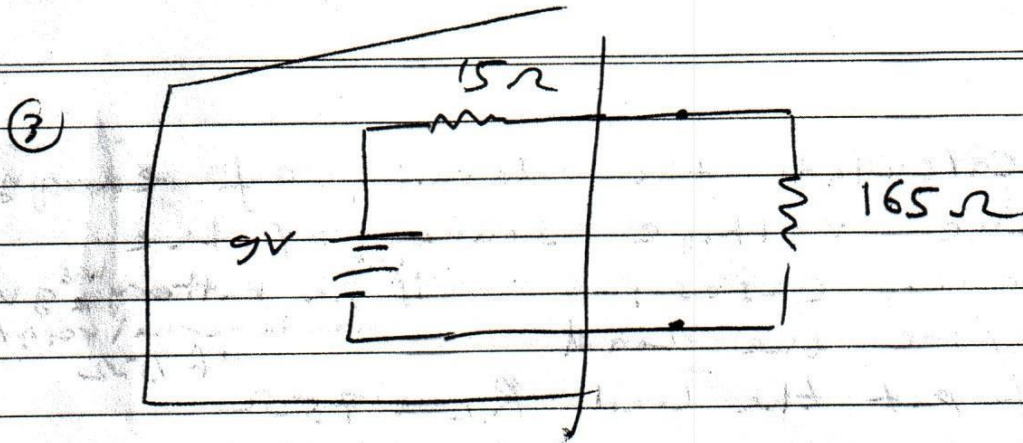That means ~~we can~~ the ^{active} usefully of from
this source not $9V$, its $7.5V$



$$I = \frac{V}{R} = \frac{9}{15 + 165} = \frac{9}{180} = 0.05 \text{ A}$$

$$V = IR = 0.05 \times 15 = 0.75 \text{ V}$$

the useful voltage only

$$\underline{\underline{8.25 \text{ V}}}$$

في المقاومة R_s نحتاج التيار

Ohms Law:

The ratio of the potential difference (V) between the ends of a conductor to the current (I) flowing between them is constant, provided the temperature do not change i.e.


$$\frac{V}{I} = \text{constant} = R$$

where R is the resistance of the conductor between the two points. If the voltage between points A and B is V volt and current flowing is I amperes, then V/I will be constant and equal to R .

The following points may be noted about ohms Law:

1. Ohms Law is true for metal conductors at constant temp., if the temp. change, Ohms Law is not applicable.
2. Ohms Law is true for d.c circuit. It is not in general valid for a.c circuits.
3. Ohms Law can be expressed in three forms:
 $I = V/R$ $V = IR$ $R = V/I$

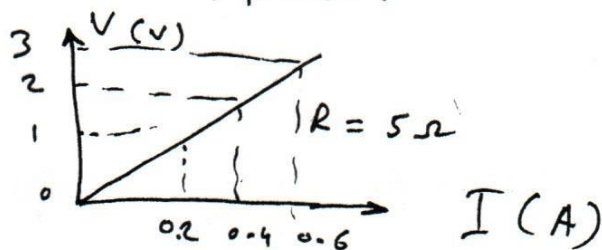4. If Ohms Law is expressed graphically (taking Voltage along Y-axis and current along X-axis) of the graph will give the resistance.




Resistances in Series:

- When some conductors having resistances R_1 , R_2 and R_3 etc. are joined end to end as in the following figure, they are said to be connected in series.

It can be proved that the equivalent resistance or total resistance between points A and D is equal to the sum of the three individual resistances.

It should be remembered that:

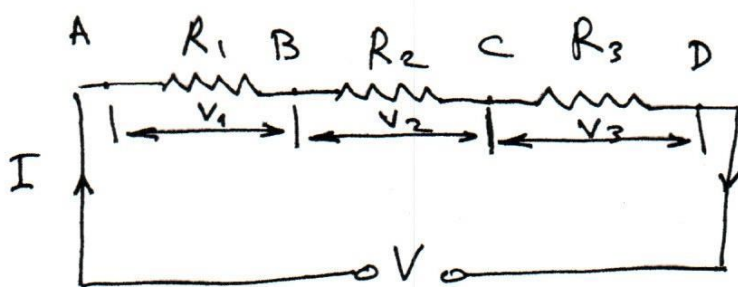- ① Current is the same through all the three conductors.
- ② Voltage drop across each is different due to its resistance and is given by ohm's law.
- ③ Sum of the three voltage drops is equal to the voltage applied across the three conductors.



$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3$$

Compensation


$$V = IR$$

$$IR = IR_1 + IR_2 + IR_3$$

$$R = R_1 + R_2 + R_3$$

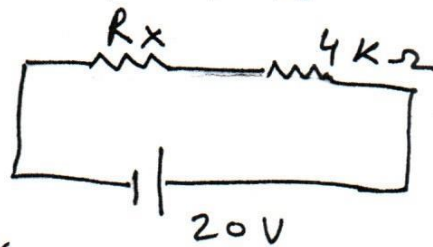(4)
Exp.

- ① Find the value of R_x who make the total current of circuit is 4 mA



Sol

total Resistance $\rightarrow R_T = \frac{V_s}{I_s} = \frac{20}{4 \text{ mA}} = 5k\Omega$


$$R_T = R_1 + R_2$$

$$5k\Omega = 4k\Omega + R_x$$

$$\therefore R_x = 1k\Omega$$

Exp

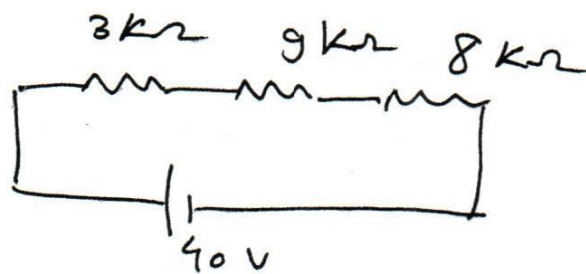Find the total resistance ~~and~~, total current and voltage each resistance for the following circuit?



Sol.

$$R_T = R_1 + R_2 + R_3$$

$$= 3 + 9 + 8 = 20k\Omega$$

$$I_t = \frac{V_s}{R_T} = \frac{40V}{20k\Omega} = 2 \text{ mA}$$

$$V_{3k\Omega} = IR = 2 \times 10^{-3} \times 3 \times 10^3 = 6V$$

$$V_{9k\Omega} = IR = 2 \times 10^{-3} \times 9 \times 10^3 = 18V$$


$$V_{8k\Omega} = IR = 2 \times 10^{-3} \times 8 \times 10^3 = 16V$$

Resistances in Parallel :

4

Three resistances, as joined in the following figure are said to be connected in parallel. In this case

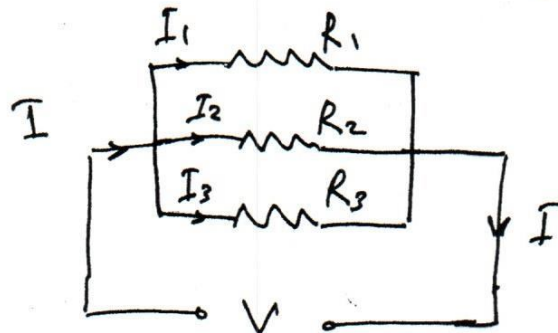- ① Potential drop across all resistances is the same
- ② Current in each resistor is different. ~~and~~
- ③ the total current is the sum of three separate current.



$$I = I_1 + I_2 + I_3$$

$$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$I = \frac{V}{R}$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad \text{or} \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or} \quad R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Ques When connect two resistors (only) in parallel the value of total resistance will be equal

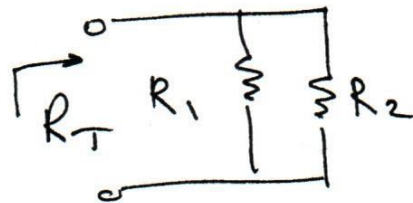
$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$



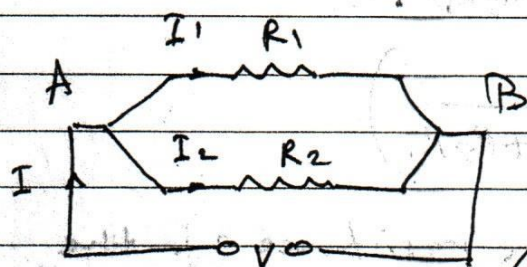(5)

Division of current in parallel Circuits:

in the following fig. two resistances are ~~joined~~ joined in parallel across a voltage V . The current in each branch, as given by ohm's Law, is



$$I_1 = V/R_1 \quad \text{and} \quad I_2 = V/R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$I = I_1 + I_2 \Rightarrow I_2 = I - I_1$$

$$\frac{I_1}{I - I_1} = \frac{R_2}{R_1} \Rightarrow I_1 R_1 = R_2 (I - I_1)$$

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2} \quad \text{and} \quad I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

Take the case of three resistors in parallel connected across a voltage V . The total current

$I = I_1 + I_2 + I_3$. Let the equivalent resistance be R . Then


$$V = IR$$

$$V = I_1 R_1 \quad IR = I_1 R_1$$

$$\frac{I}{I_1} = \frac{R_1}{R} \quad \text{or} \quad I_1 = IR/R_1 \quad \text{--- (1)}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
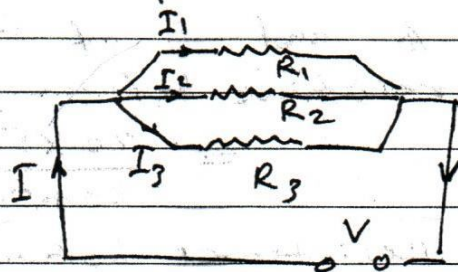
$$R = \frac{R_1 R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2}$$




From \rightarrow ①

$$I_1 = I \left(\frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$$

Similarly $I_2 = I \left(\frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$ and

$$I_3 = I \left(\frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$$

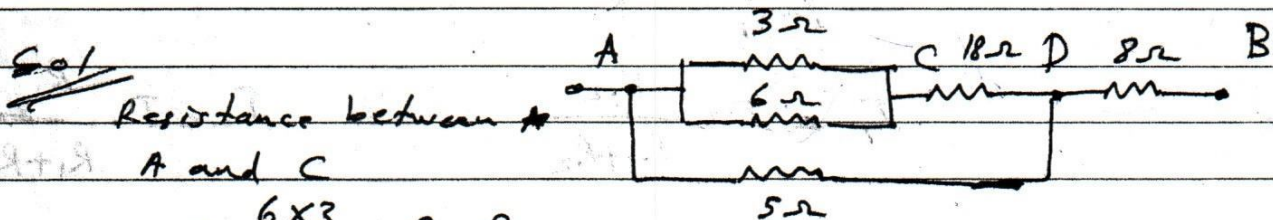Exp. Calculate the effective resistance of the following combination of resistances and the voltage drop across each resistance when a potential drop of (60 V) is applied between points A and B



$$= \frac{6 \times 3}{6 + 3} = 2 \Omega$$

Resistance of branch ACD

$$= 18 + 2 = 20 \Omega$$

Now there are two parallel paths between points A and D of resistance (20 Ω) and (5 Ω)
Hence, resistance between A and D

$$= \frac{20 \times 5}{20 + 5} = 4 \Omega$$

\therefore Resistance between A and B = 4 + 8 = 12 Ω

total current = 60/12 = 5 A

Current through 5 Ω resistor = $5 \times \frac{20}{25} = 4$ A $\left(I_{(R_1)} = I_t \times \frac{R_1}{R_1 + R_2} \right)$

in branch ACD = $5 \times \frac{5}{25} = 1$ A

P.D. across 3 Ω and 6 Ω resistors = $1 \times 2 = 2$ V

" " 18 Ω resistor = $18 \times 1 = 18$ V


" " 5 Ω " = $5 \times 4 = 20$ V

" " 8 Ω " = $8 \times 5 = 40$ V

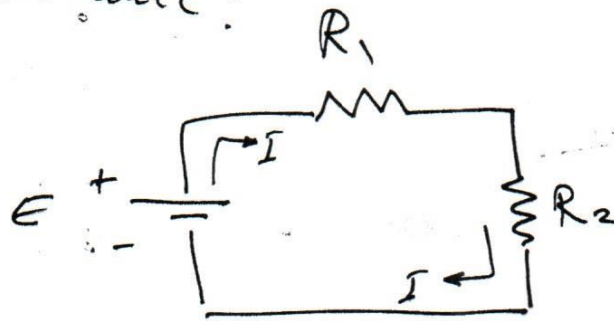(6)

Voltage division law

The following figure as shown two series resistance:



We can write this relationship:

$$R_t = R_1 + R_2$$

$$E = I \cdot R_t = I \cdot (R_1 + R_2)$$

$$I = \frac{E}{R_1 + R_2}$$

Compensation in values of current we obtain

$$V_1 = I \cdot R_1 = E \times \frac{R_1}{R_1 + R_2}$$

$$V_2 = I \cdot R_2 = E \times \frac{R_2}{R_1 + R_2}$$


This relationship acts the relation voltage division in the electric circuits when contains of series resistances.

Exp.

Calculate the total current and the voltage on the leads of each resistance and the voltage between C, b for the following electric circuit

Sol

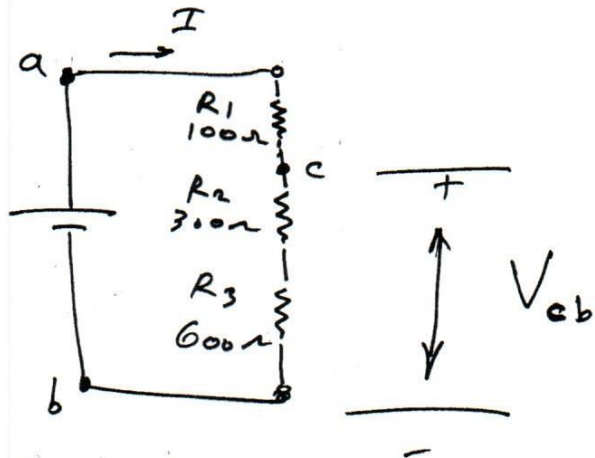- ① We solve this
Exp. using ~~Karman's law~~
Ohm's law:



$$R_t = R_1 + R_2 + R_3 = 100 + 300 + 600 = 1000 \Omega$$

$$I_t = \frac{E(V)}{R_t} = \frac{10}{1000} = 0.01 A = 10 \text{ mA}$$

$$V_1 = I R_1 = 0.01 \times 100 = 1V$$

$$V_2 = I R_2 = 0.01 \times 300 = 3V$$

$$V_3 = I R_3 = 0.01 \times 600 = 6V$$

$$\therefore E = V_1 + V_2 + V_3 = 10V$$

$$V_{cb} = I \times (R_2 + R_3) = 0.01 \times (300 + 600) = 9V$$

- ② Sol. Exp using Voltage division Law:

$$V_1 = E \times \frac{R_1}{R_1 + R_2 + R_3} = 10 \times \frac{100}{1000} = 1V$$

$$V_2 = E \times \frac{R_2}{R_1 + R_2 + R_3} = 10 \times \frac{300}{1000} = 3V$$

$$V_3 = E \times \frac{R_3}{R_1 + R_2 + R_3} = 10 \times \frac{600}{1000} = 6V$$

$$V_{cb} = E \times \frac{R_2 + R_3}{R_1 + R_2 + R_3} = 10 \times \frac{900}{1000} = 9V //$$

Atomic Theory

All materials consist of very small atoms, the atom consists of two general parts:

① It has a hard central core known as nucleus. It contains two types of particles; one is known as proton and carries positive charge, the other is neutron which is electrically neutral.

② Revolving round.

Coulomb Law :

The fundamental unit for charge is Coulomb

$$F = K \frac{Q_1 Q_2}{r^2}$$

F - the force between charges, its unit (N)

Q_1, Q_2 - the charges, its unit (C) [$Q = 1.6 \times 10^{-19} \text{ C}$]

r - The distance between the two charges, its unit (m)

K - Coulomb's constant and equal $9 \times 10^9 \text{ m}^2 \cdot \text{N} / \text{C}^2$

Exp. If was the attraction force between two charges 100N, Now how much become the force between them if multiply the distance between them?

Sol First case:

$$F_1 = K \frac{q_1 q_2}{r_1^2} = 100$$

second case:

$$F_2 = K \frac{q_1 q_2}{(2r_1)^2}$$

by dividing $\frac{F_1}{F_2}$ we obtain:

$$\frac{F_1}{F_2} = \frac{K \frac{q_1 q_2}{r_1^2}}{K \frac{q_1 q_2}{(2r_1)^2}} = \frac{4r_1^2}{r_1^2} = \underline{4}$$

That's mean the force in second case its $(\frac{1}{4})$ from value of first force.

$$\therefore F_2 = \frac{1}{4} F_1 = \frac{1}{4} \times 100 = 25N$$

we see the force decreased when the distance its increased.

Classification of materials (The force will be decreased by increasing of distance)

- (1) Conductors
- (2) Dielectric
- (3) Semi-conductors

Electrical current:

< II

The el. current has known the beam of electr. in the conductor and its unit Ampere (A). and we can to define the elec. current as the average of charge changing cross unit of time:

$$\bar{I} = \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} \quad (C/s).$$

• Types of current:

- ① Direct current
- ② Alternative current

The density of current (J)

$$J = \frac{I}{S} \quad A/mm^2$$

• The electro-motive force (emf):

The ^{power} ~~energy~~ who very important to carry the charge between two Nodes and its symbol (V) & unit volt.

$$V = \frac{P}{I}$$

$$P = V \times I$$

$$1V = \frac{1 \text{ Watt}}{1 \text{ ampere}}$$

The relation ship between the resistance, length of conductor and area of section.

$$R = \rho \frac{l}{A}$$

R - resistance (Ω)

l - conductor length (m)

A - area of section for conductor (m^2)

ρ - Resistivity ($\Omega \cdot m$)

Exp.

Conductor of copalt cylinder has length 50m and the ~~length~~ Radius of section its 2mm.

Calculate the resistance of this conductor if you know the quality resistance of copalt its $2.7 \times 10^{-8} \Omega \cdot m$

Sol

$$A = \pi r^2$$

$$= \pi (2 \times 10^{-3})^2 = 1.26 \times 10^{-5} m^2$$

$$R = \rho \frac{l}{A}$$

$$= 2.7 \times 10^{-8} \frac{50 \times 10^3}{1.26 \times 10^{-5}} = 107 \Omega$$

III

The effect of temperature on
the resistance

$$R_1 = R_0 (1 + \alpha (T_1 - T_0))$$

R_1 - The value of resistance on finally temp T_1
(Ω)

R_0 - The value of resistance on primary temp T_0
(Ω)

T_1 - The finally temperature ($^{\circ}\text{C}$)

T_0 - The primary temp. ($^{\circ}\text{C}$)

α - The quality temperature for the material
($1/^{\circ}\text{C}$)

Exp.

The value of carbon resistance in the begin
of cycle (temperature 20°C) was (15Ω)

calculate its value when the temp. become

(70°C). The quality temp. for carbon $\alpha = 0.004/^{\circ}\text{C}$

Sol

$$R_1 = R_0 (1 + \alpha (T_1 - T_0))$$

$$= 15 (1 + 0.004 (70 - 20))$$

$$= 15 \times 1.2 = 18\Omega$$

The conductivity :

$$(5) G = \frac{1}{R} \quad \Omega^{-1} \Rightarrow G = \frac{\mu \times A}{L}$$

μ - The quality conductivity

The power :

$$\begin{aligned} P &= IV \\ &= I^2 R \\ &= \frac{V^2}{R} \end{aligned}$$

The efficiency

$$\eta = \frac{P_{out}}{P_{input}} \times 100\%$$

unit less

V - Volt drop (V)
I - current (A)
R - resistance (Ω)
P - Power (W)

The Energy :

$$E = P \cdot t$$

E - energy (J)
P - Power (W)
T - time (s)

Exo Find the energy (dissipation) by cause the working of instrument his power 1800 W for one hour ?

Sol For measuring the power by unit joule or watt we must first to convert the time from hour to seconds

$$t = 1 \times 60 \times 60 = 3600 \text{ s}$$

$$E = Pt = 1800 \times 3600 = 6480 \text{ Kw.s}$$

OR

$$E = Pt = 1.8 \times 1 = 1.8 \text{ Kw.h}$$

Classification of Elements :

The circuit element can be classified as:

1. Linear element: if the voltage-current characteristic is a straight line.

2. Non Linear element: if the relationship between voltage and current is not a straight line.

3. Passive element: is an element containing no sources of energy such as resistance, inductance and capacitance.


4. Active element: is an element having internal energy source such as generator, battery.

Voltage and Current sources


The two very important sources (active elements) are:

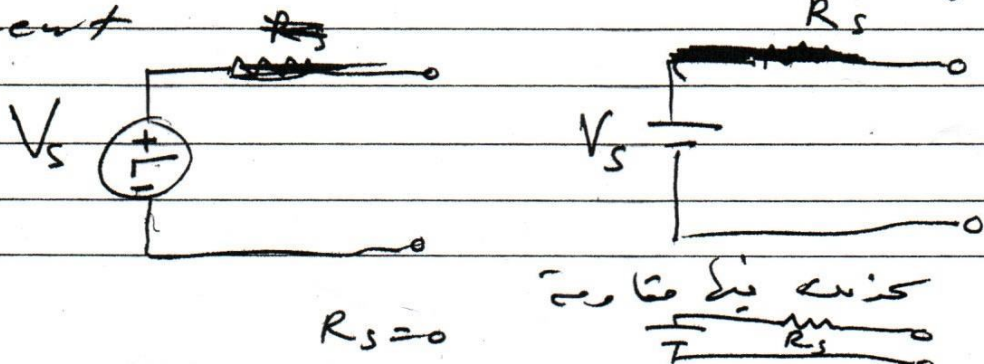1. independent voltage source
2. independent current source


① An independent voltage source is a two terminal such as a battery or a generator. The voltage is independent of the current through the element.



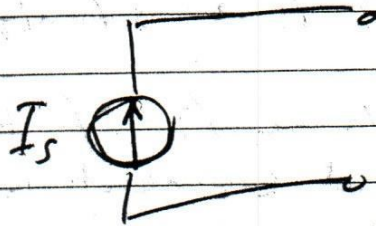② An independent current source is a two terminal element through which a current flows. The current is independent of the voltage across the element.



پروجیکٹ سٹارٹ دیا گیا ہے

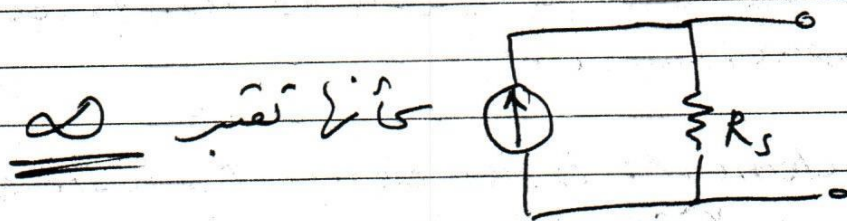

Exp

① Change the 300 mH to H

$$300 \text{ mH} = \frac{300}{10^3} = 0.3 \text{ H}$$

② Change the 47000 Ω to M Ω

$$47000 \Omega = \frac{47000}{10^3 \times 10^3} = 0.047 \text{ M}\Omega$$

③ Find the total resistance for the following series resistances?

$$R_1 = 30 \text{ K}\Omega \quad R_2 = 0.04 \text{ M}\Omega \quad R_3 = 5600 \Omega$$

$$R_2 = 0.04 \text{ M}\Omega = 0.04 \times 10^3 = 40 \text{ K}\Omega$$

$$R_3 = 5600 \Omega = \frac{5600}{10^3} = 5.6 \text{ K}\Omega$$

$$R_1 + R_2 + R_3 = 30 \text{ K} + 40 \text{ K} + 5.6 \text{ K} \\ = 75.6 \text{ K}\Omega$$

④ Find the total capacitance for the parallel capacitance

$$C_1 = 0.0002 \text{ mF} \quad C_2 = 0.1 \mu\text{F} \quad C_3 = 10000 \text{ pF}$$

$$C_1 = 0.0002 \text{ mF} = 0.0002 \times 10^3 = 0.2 \mu\text{F}$$

$$C_3 = 10000 \text{ pF} = \frac{10000}{10^3 \times 10^3} = 0.01 \mu\text{F}$$


$$C_1 + C_2 + C_3 = 0.2 \mu + 0.01 \mu + 0.1 \mu = 0.31 \mu\text{F}$$

EXP

Calculate the potential between the ideal current source (10 mA) if the load:


1. $5\text{ k}\Omega$
2. $2\text{ k}\Omega$

①

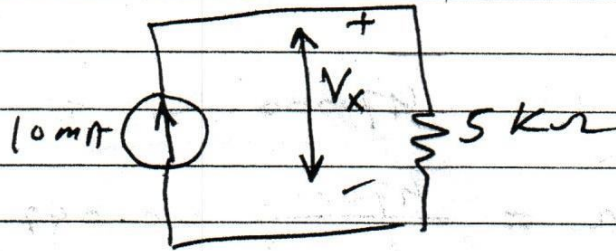

$$V_x = IR$$
$$= 10 \times 10^{-3} \times 5 \times 10^3 = 50\text{ V}$$

②


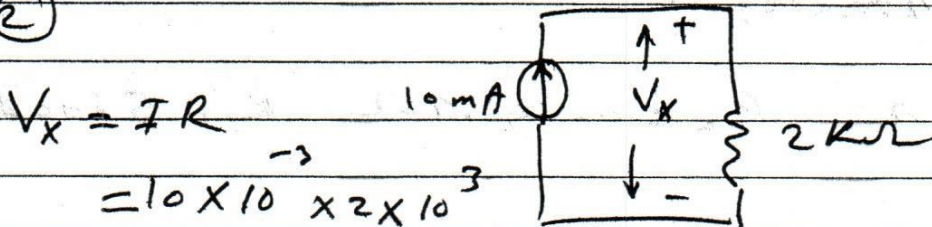


$$V_x = IR$$
$$= 10 \times 10^{-3} \times 2 \times 10^3$$
$$= 20\text{ V}$$


We can see how the potential is changing when we change the load but the current stay without changing

⑦ The Convention laws from delta to star in the electrical circuits.

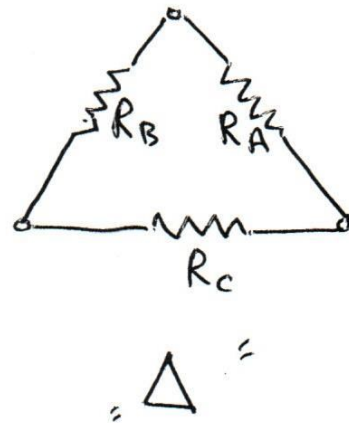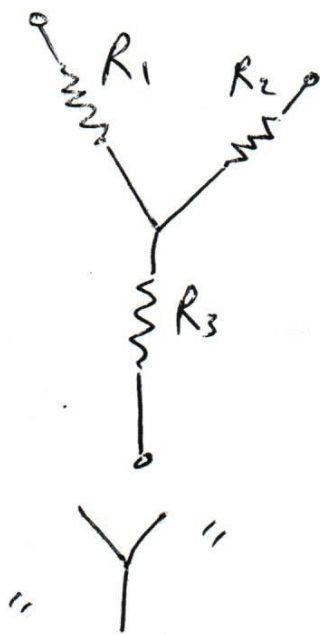
The following fig. showing three resistances R_A, R_B, R_C connected as delta, and three resistances R_1, R_2, R_3 connected as star.



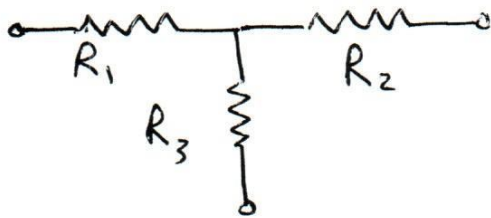We can to simplified these figures as different figures:




Connection T

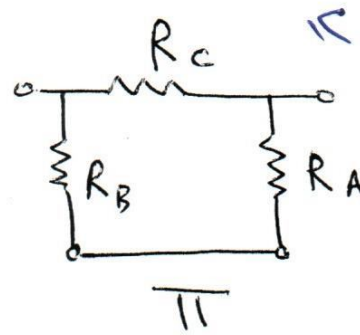

connection Π

① Star/delta Transformation

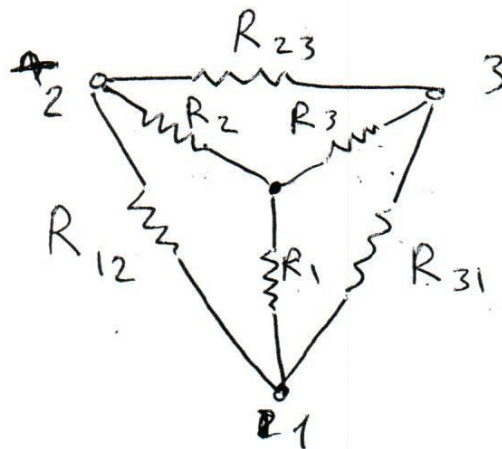Easy we can ~~use base~~ simplify this base as :



$$R_{31} = \frac{R_2 R_3 + R_1 R_2 + R_1 R_3}{R_2}$$

$$R_{12} = \frac{R_2 R_3 + R_1 R_2 + R_1 R_3}{R_3}$$



$$R_{23} = \frac{R_2 R_3 + R_1 R_2 + R_1 R_3}{R_1}$$



② Delta/star Transformation

If we have complicated networks can be simplified by successively replacing delta meshes by equivalent star systems and vice versa.

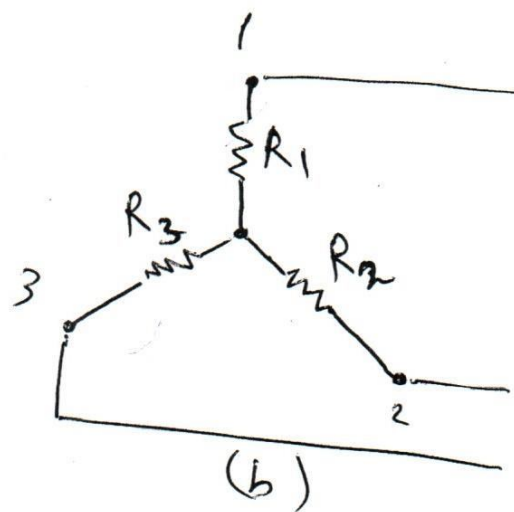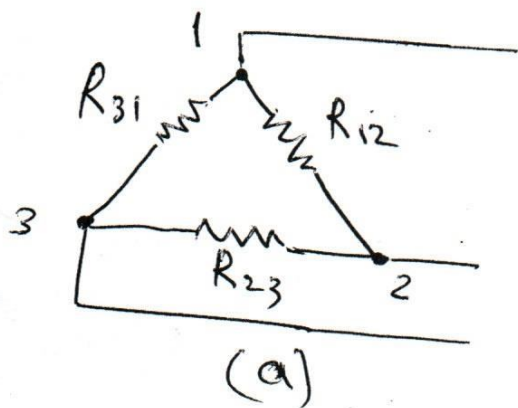Suppose we are given three resistances R_{12}, R_{23}, R_{31} connected in delta fashion between terminal 1, 2 and 3 as in the following Fig.(a). So far as the respective terminals are connected these three resistances can be replaced by the three resistances R_1, R_2 and R_3 connected in star as in Fig.(b).



These two arrangements will be electrically equivalent if the resistance as measured between any pair of terminals is the same in both the arrangements. Let us find this condition.

First, take delta connection: between terminals 1 and 2, there are two parallel paths; one having

a resistance of R_{12} and other having a resistance of $(R_{23} + R_{31})$.

∴ Resistance between terminals 1 and 2 is:

$$\frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})}$$

Now take the star connection: The resistance between the same terminals 1 and 2 is $(R_1 + R_2)$. As terminal resistances have to be the same

$$R_1 + R_2 = \frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (1)}$$

Similarly, for terminals 2 and 3 and terminal 3 and 1, we get:

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

$$R_3 + R_1 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (3)}$$


Now subtracting (2) from (1) and adding the result to (3), we get:

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}; R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}; R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

9

EXA. 1

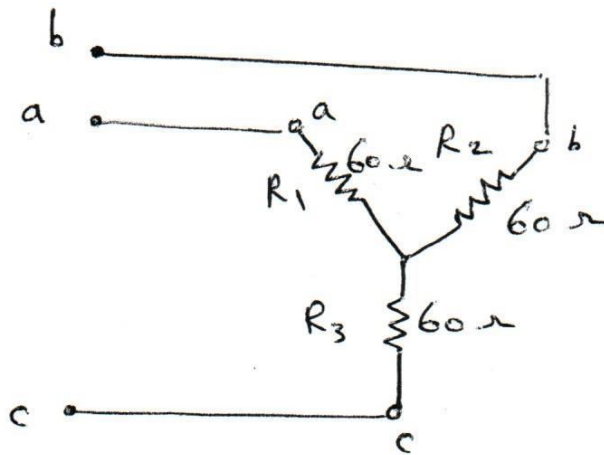For the following circuit convert the connection of star to delta?



Sol

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_A = \frac{60 \times 60 + 60 \times 60 + 60 \times 60}{60} = 180 \Omega$$

$$R_A = R_B = R_C = 180 \Omega$$


The ~~connection~~ resistances of star connection its equal,

\therefore we can calculate the value of resistances in delta connection by direct equation:

$$R_\Delta = 3 \times R_Y = 3 \times 60 = 180 \Omega$$


and the equivalent circuit:



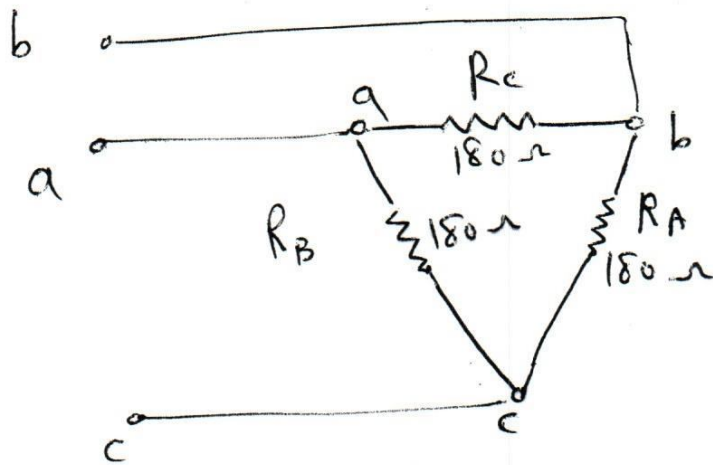

EXP. 2

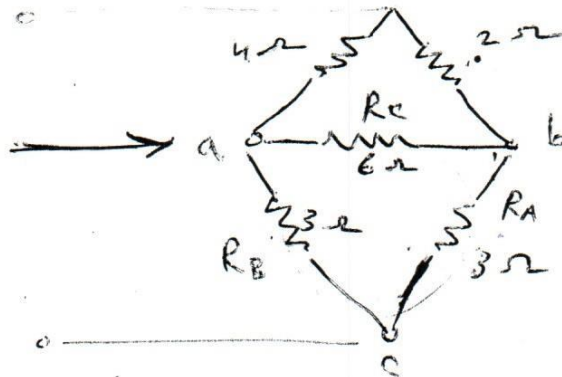
Calculate the equivalent resistance for the following circuit:



Sol/ Convert the delta connection for resistances (R_A, R_B, R_C) to the star connection.
 As shown in the circuit has two equal resistances in the delta connection, that means we will get two equal resistances in the star connection;

$$R_1 = R_2 = \frac{3 \times 6}{3 + 3 + 6} = 1.5\ \Omega$$

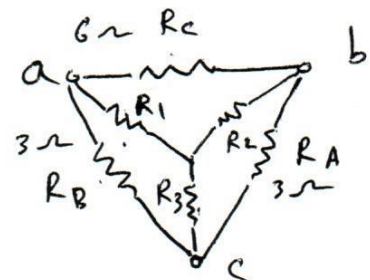
$$R_3 = \frac{3 \times 3}{12} = 0.75\ \Omega$$



— —

10

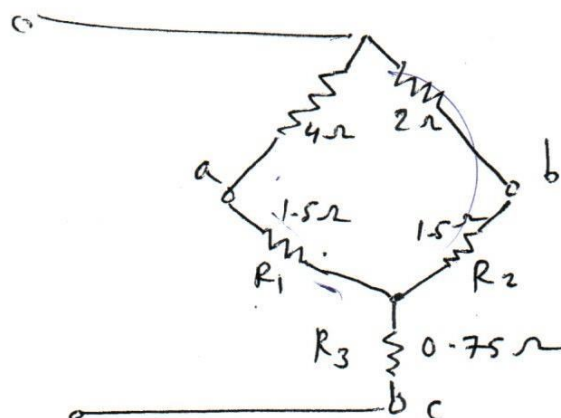The electric circuit will be as the following circuit:




and calculate the equivalent resistance for this circuit from the equation:

$$R_{eq} = 0.75 + \frac{(4+1.5)(2+1.5)}{(4+1.5) + (2+1.5)} = 2.889 \Omega$$

Exp. 3

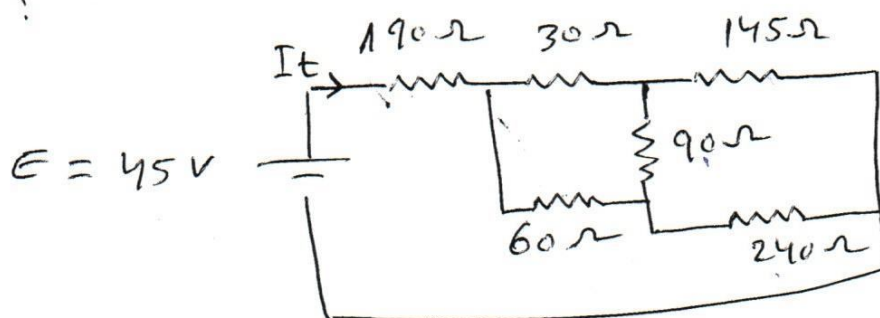Calculate the total current in the following circuit:



Sol/

We can see more than one method for finding the total equivalent resistance.

- ① considerate the resistances (90, 145, 240) are connected in delta connection and convert to star.
- ② considerate the resistances (30, 145, 90) and

(60, 90, 240) as star connection and convert to Δ connection.


but we take the resistances (60, 30, 90) as Δ connection and convert to star connection:

$$R_A = \frac{30 \times 90}{30 + 90 + 60} = 15 \Omega$$

$$R_B = \frac{90 \times 60}{30 + 90 + 60} = 30 \Omega$$

$$R_C = \frac{30 \times 60}{30 + 90 + 60} = 10 \Omega$$

The circuit will be :

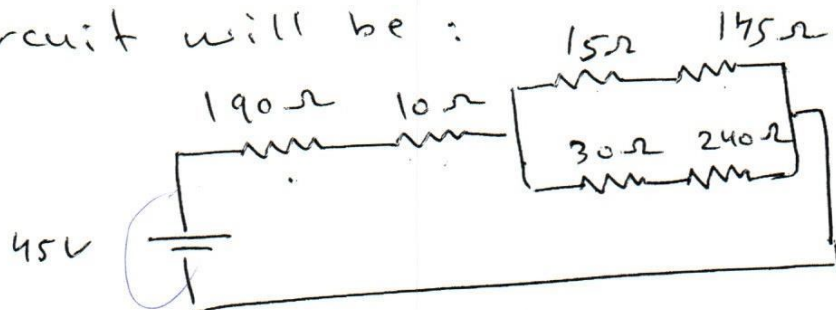


The resistances (15, 145) in series connection and the resistances (30, 240)

$$30 + 240 = 270 \Omega$$

$$15 + 145 = 160 \Omega$$

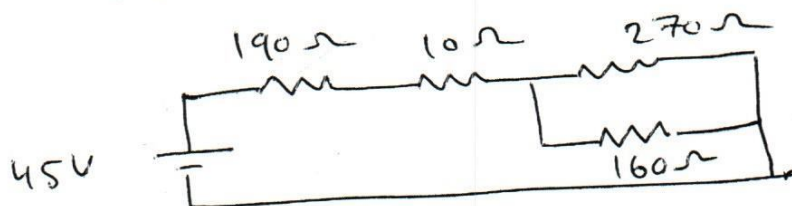and the last resistances in parallel connection?



$$270 // 160 = \frac{270 \times 160}{270 + 160} = 100 \Omega$$

The Total equivalent resistance:

$$R_T = R_1 + R_2 + R_3 = 190 + 10 + 100 = 300 \Omega$$

\therefore


$$I_t = \frac{V_T}{R_T} = \frac{45}{300} = 0.15 \text{ A}$$

11) Exp. 4


Find the total current for the following circuit,

$$R_1 = 6\Omega, R_2 = 12\Omega, R_3 = 9\Omega, R_4 = 6\Omega, R_5 = 5\Omega, R_6 = 10\Omega$$
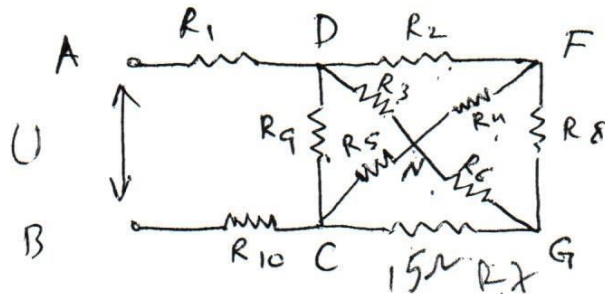
$$R_7 = 15\Omega, R_8 = 10\Omega, R_9 = 15\Omega, U = 57V, R_{10} = 15\Omega$$



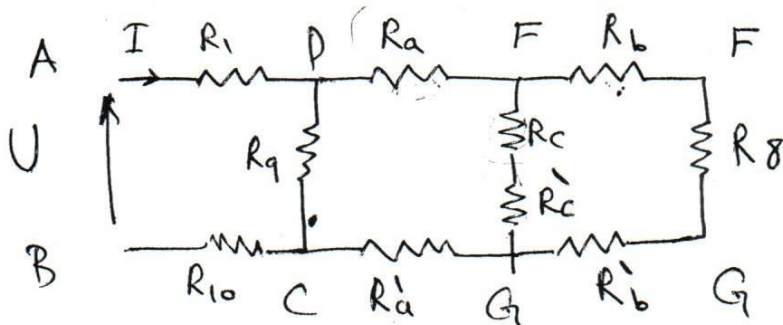Sol/ By converting the delta connection between NFDN and NCGN to star connection we get the following circuit:



$$R_a = \frac{R_2 \cdot R_3}{R_4 + R_2 + R_3} = \frac{12 \times 9}{12 + 9 + 6} = 4\Omega$$

$$R_b = \frac{R_2 \cdot R_4}{R_4 + R_2 + R_3} = \frac{12 \times 9}{12 + 9 + 6} = \frac{8}{3} = 2.667\Omega$$

$$R_c = \frac{R_3 \cdot R_4}{R_4 + R_2 + R_3} = \frac{6 \times 9}{12 + 9 + 6} = 2\Omega$$


$$R'_a = \frac{R_5 \cdot R_7}{R_5 + R_7 + R_6} = \frac{15 \times 5}{30} = 2.5 \Omega$$

17

$$R'_b = \frac{R_6 \cdot R_7}{R_6 + R_7 + R_5} = \frac{10 \times 15}{30} = 5 \Omega$$

$$R'_c = \frac{R_5 \cdot R_6}{R_5 + R_6 + R_7} = \frac{5 \times 10}{30} = 1.6667 \Omega$$
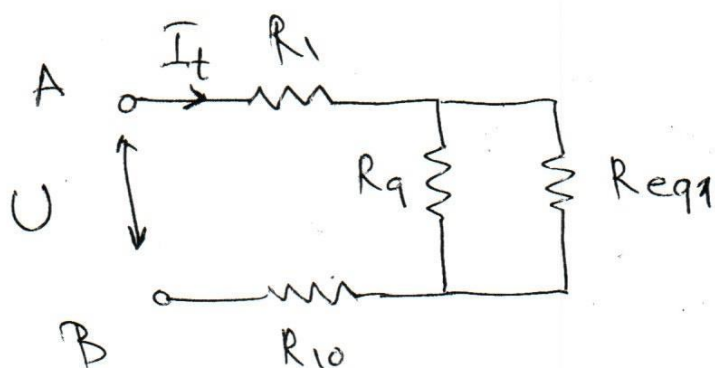
$$R_{eq1} = \frac{(R_b + R'_b + R_8)(R_c + R'_c)}{(R_b + R'_b + R_8) + (R_c + R'_c)} + (R_a + R'_a) = 15 \Omega$$



$$R_{eq} = R_1 + R_{10} + \frac{(R_9 \cdot R_{eq1})}{R_9 + R_{eq1}} = 28.5 \Omega$$

$$I_t = \frac{U}{R_{eq}} = \frac{57}{\frac{27.5}{28.5}} = 2 A$$

(12) LRU

Kirchhoff's Laws

By the middle of the nineteenth century a considerable amount of experience with electric circuits had been gained by the leading men of science of that time. However, it was Gustav Robert Kirchhoff (1824 - 1887) who published the first systematic formulation of the principles governing the behaviour of electric circuits. He advanced no new experimental facts or concepts but merely restated familiar principles. His work was embodied in two laws - a current and a voltage law - which together are known as Kirchhoff's laws. It is upon these laws that electric circuit theory is based. These laws are used (a) in determining the equivalent resistance of a complicated network of conductors and (b) for calculating the currents flowing in the various conductors. The two laws can be defined as:

1- Kirchhoff's Current Law (KCL)

It states as follows:

«In any electrical network, the algebraic sum of the currents meeting at a point (or junction) is zero».

14


put in another way, it simply means that the total current leaving a junction is equal to the total current entering that junction. It is obviously true because there is no accumulation of charge at the junction of the network.

Consider the case of a few conductors meeting at a point A as in figure. Some conductors have currents leading to point A, whereas some have current leading away from point A. Assuming the incoming currents to be positive and the outgoing currents negative, we have:

$$I_1 + (-I_2) + (-I_3) + (+I_4) + (-I_5) = 0$$

$$I_1 + I_4 - I_2 - I_3 - I_5 = 0 \quad \text{or} \quad I_1 + I_4 = I_2 + I_3 + I_5$$

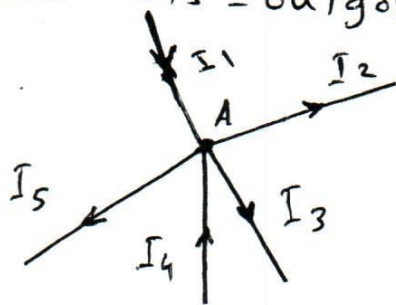
or incoming currents = outgoing currents.



Similarly, in figure for node A:

$$+I + (-I_1) + (-I_2) + (-I_3) + (-I_4) = 0 \quad \text{or} \quad I = I_1 + I_2 + I_3 + I_4$$

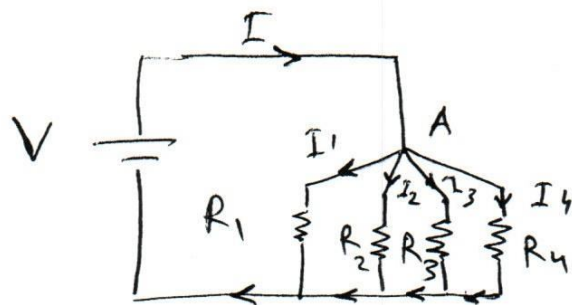We can express the above conclusion thus: $\sum I = 0$ at a junction.




(13)

2- Kirchhoff's Voltage Law (KVL)

It states as follows:

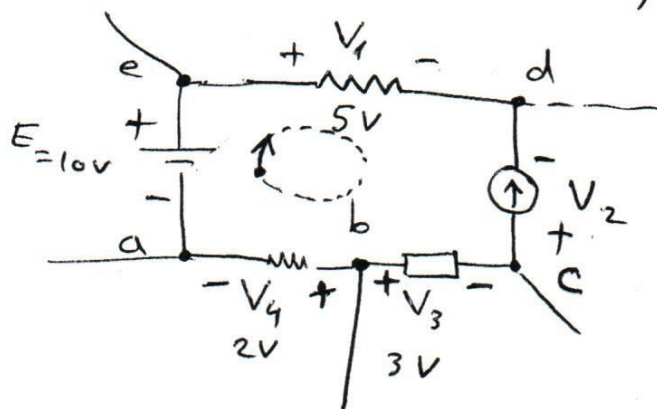a) The algebraic sum of the products of currents and resistances is each of the conductors in any closed path (or mesh) in a network plus the algebraic sum of the e.m.f.s. in that path is zero.


In other words, $\sum IR + \sum \text{e.m.f.} = 0$ round a mesh



$$E - V_1 + V_2 + V_3 - V_4 = 0$$

$$E + V_2 + V_3 = V_1 + V_4$$

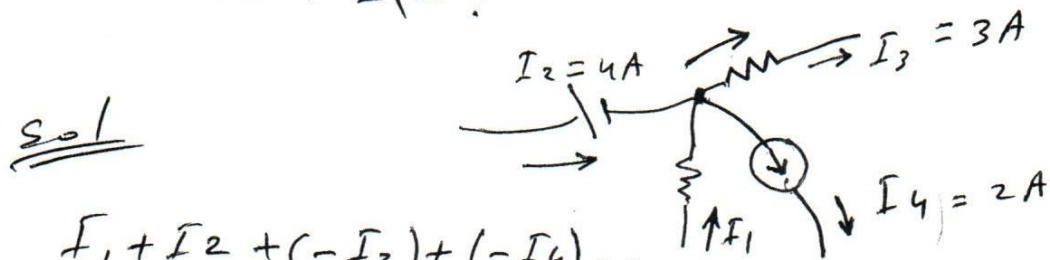EXP. write the KCL for currents of node shown of the following Fig. ? Calculate the current $I_1 = ?$




$$I_1 + I_2 + (-I_3) + (-I_4) = 0$$

$$I_1 + I_2 = I_3 + I_4$$

$$I_1 = I_3 + I_4 - I_2 = 3 + 2 - 4 = \underline{\underline{1A}}$$

Exp.

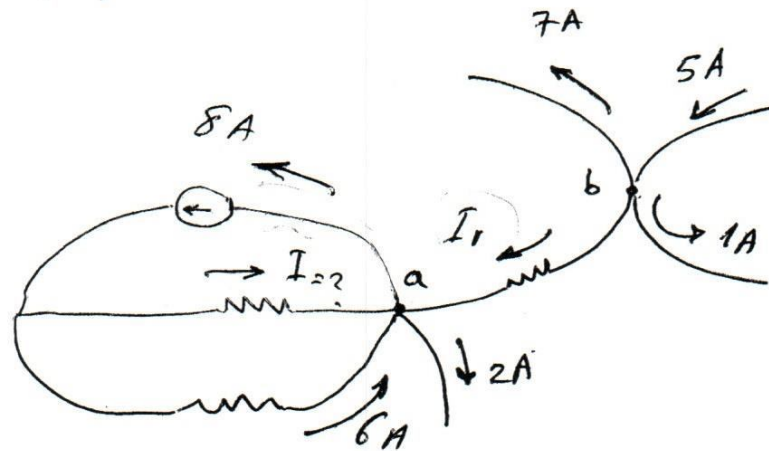Calculate the current $I = ?$ for the following circuit:



Sol

Node b


$$5 = 7 + 1 + I_1 \Rightarrow I_1 = 5 - 8 = -3A$$

Node a

$$I + 6 + I_1 = 8 + 2 \Rightarrow \underline{I} = 10 - 6 - I_1 = 7A$$

Exp

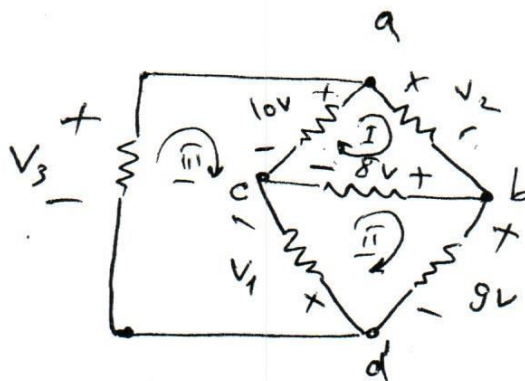calculate the Voltages V_1, V_2, V_3 for the following circuit:



First Loop I

$$10 - V_2 - 8 = 0 \Rightarrow V_2 = 10 - 8 = 2V$$

Second Loop II

$$-V_1 + 8 - 9 = 0 \Rightarrow V_1 = 8 - 9 = -1V$$

Third Loop III


$$V_3 - 10 + V_1 = 0 \Rightarrow V_3 = 10 - V_1 = 10 - (-1) = 11V$$

(14)

Exp.

19

By using Kirchhoff's laws calculate the values of currents I_1, I_2, I_3 for the following circuit:

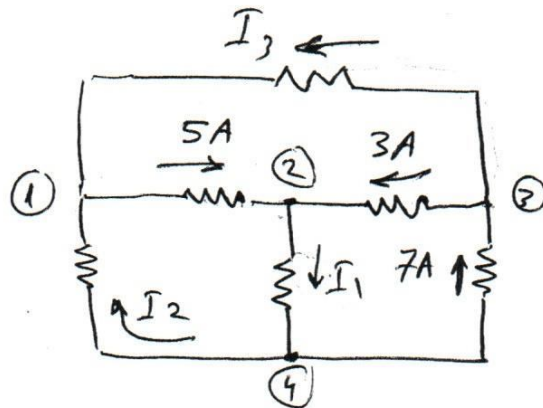Sol

In the node ① has two unknown current and in the nodes 2, 3 has one ~~unknown~~ unknown current, at least we will begin in the node ②:

$$I_1 = 5 + 3 = 8A$$


Node ③

$$7 = 3 + I_3 \Rightarrow I_3 = 7 - 3 = 4A$$

Node ①

$$I_2 + I_3 = 5 \Rightarrow I_2 = 5 - I_3 = 5 - 4 = 1A$$

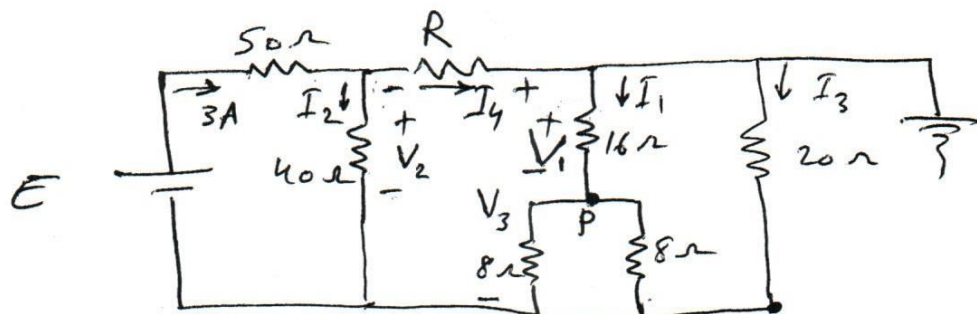Exp. If the voltage of Point (P) at the following circuit equal $V_P = -16V$, Calculate each of R, E .



Sol The voltage of point (P) equal (-16V) :

$$\therefore V_1 = 16V$$

and the value of current :

$$I_1 = \frac{V_1}{16} = \frac{16}{16} = 1A$$

and the equivalent resistance for the branch of wire contain the point (P) equal

$$R_{eq1} = 16 + \frac{8 \times 8}{8+8} = 16 + 4 = 20\Omega$$

$$\therefore V_3 = 1 \times R_{eq1} = 1 \times 20 = 20V$$

$$I_3 = \frac{V_3}{20} = \frac{20}{20} = 1A$$

and using the KCL we obtained :

$$I_4 = I_1 + I_3 = 1 + 1 = 2A$$

$$\text{KCL at } I_2 + I_4 = 3 \Rightarrow I_2 = 3 - I_4 = 3 - 2 = 1A$$

$$V_2 = I_2 \times R_0 = 1 \times 40 = 40$$

The drop voltage on the leads of resistance equal :


$$V_R = V_2 - V_3 = 40 - 20 = 20V$$

$$\therefore R = \frac{V_R}{I_4} = \frac{20}{2} = 10\Omega$$

by using KVL we obtained :

$$E = 3 \times 50 + V_2 = 150 + 40 = 190V$$

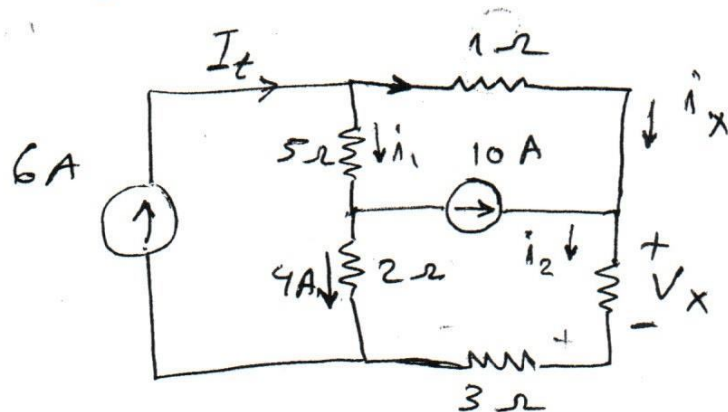(15) Find the value of i_x , V_x in the following circuit?



Sol ① By using KCL we obtained the values of current i_x :

$$i_1 = 4 + 10 = 14 \text{ A}$$

$$I_t = i_1 + i_x$$

$$6 = 14 + i_x \Rightarrow i_x = -8 \text{ A} \Rightarrow 10 + (-8) = i_2$$

$i_2 = 2 \text{ A}$


② By using KVL we obtained the values of V_x :

$$(4 \times 2) + (5 \times 14) - (-8 \times 1) - V_x - (3 \times 2) = 0$$


$$8 + 70 + 8 - 6 = V_x \Rightarrow V_x = 80 \text{ V}$$

EXP

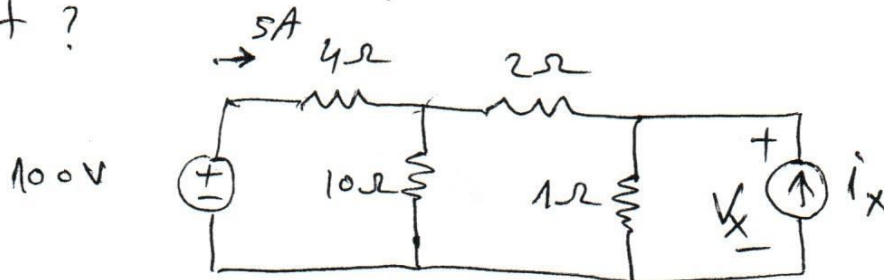Find the value of i_x , V_x for the following circuit?



Sol

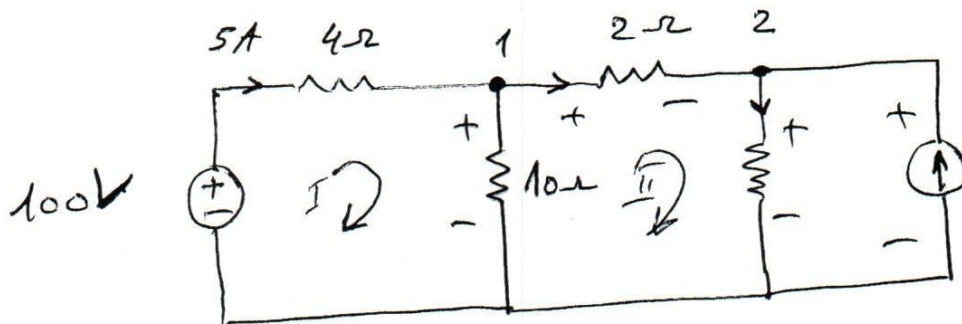

~~100 - 5 \times 4 - V_{10\Omega} = 0~~

$$V_{10\Omega} = 100 - 20 = 80V$$

$$I_{10\Omega} = \frac{V_{10\Omega}}{10} = \frac{80}{10} = 8A$$

we see the node 1 :

$$5 = 8 + I_{2\Omega} \Rightarrow I_{2\Omega} = -3A$$

$$V_{2\Omega} = I_{2\Omega} \times R = (-3) \times 2 = -6V$$

By using KVL on the second loop II we obtained :

$$V_{10\Omega} - (-6) + V_{1\Omega} = 0 \Rightarrow 80 + 6 = V_{1\Omega} \Rightarrow V_{1\Omega} = 86V$$

$$I_{1\Omega} = \frac{V_{1\Omega}}{1} = 86A$$

Both of the resistor (1Ω) and the current source (V_x) are connected in parallel :

$$\therefore V_x = V_{1\Omega} = 86V$$

By using KCL on the node 2 for obtaining the value of I_x :

$$I_{2\Omega} + I_x = I_{1\Omega}$$

$$-3 + I_x = 86$$


$$I_x = 89A$$

(16)

Circuit Analysis by Using Kirchhofs laws.

The Kirchhofs current law its active for each Node, and Kirchhofs voltage law its active for each loop in it. we can to analysis electric circuit by considering vector of branch current by using Kirchhofs laws for obtaining on the number of equation equal to number of unknown currents.

Exp.

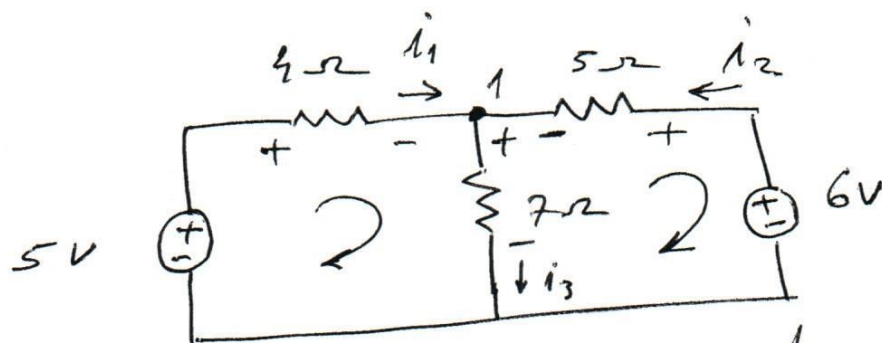

By using Kirchhof law for current on the first node 1:

$$\sum I_{in} = \sum I_{out}$$
$$i_1 + i_2 = i_3 \quad \text{--- (1)}$$

By using Kirchhof law for voltage on the both of loops:

$$+5 - V_{4\Omega} - V_{7\Omega} = 0$$
$$5 - 4i_1 - 7i_3 = 0 \quad \text{--- (2)}$$

$$V_{7\Omega} + V_{5\Omega} - 6 = 0$$

$$7i_3 + 5i_2 - 6 = 0 \quad \text{--- (3)}$$

By substituting value of i_3 from eq. (1) to eq. (2) and (3) we obtained:

$$6 - 7(i_1 + i_2) - 5i_2 = 0$$

$$6 - 7i_1 - 7i_2 - 5i_2 = 0$$

$$-7i_1 - 12i_2 = 0$$

$$7i_1 + 12i_2 = 6 \quad \text{--- (4)}$$

$$-5 + 4i_1 + 7(i_1 + i_2) = 0$$

$$-5 + 4i_1 + 7i_1 + 7i_2 = 0$$

$$11i_1 + 7i_2 = 5 \quad \text{--- (5)}$$


by solving eq. (4) and (5) we obtained:

$$i_2 = 0.37 \text{ A} \quad i_1 = 0.22 \text{ A}$$

$$i_3 = i_1 + i_2 = 0.22 + 0.37 = 0.59 \text{ A}$$

EXP.

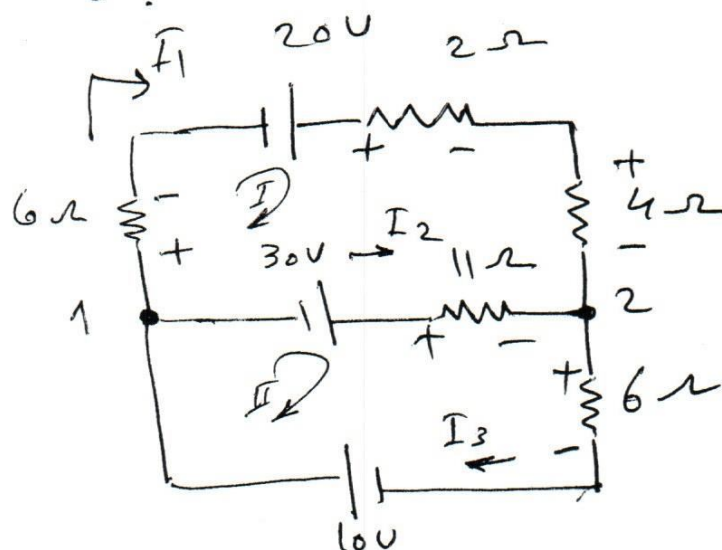In the circuit shown below, determine the direction value of currents in each of the batteries.



(17)

- انکس حل سوال

Sol

$$\underline{\underline{I_3 = I_2 + I_1}} \quad \text{--- (1)}$$

AT nodes 1, 2

AT Loops (I, II)

$$20 - 12 I_1 + 11 I_2 - 30 = 0$$

$$-12 I_1 + 11 I_2 = -10$$

$$12 I_1 - 11 I_2 = -10 \quad \text{--- (2)}$$

$$40V - 11 I_2 - 6 I_3 = 0$$

$$-11 I_2 - 6 I_3 = -40$$

$$11 I_2 + 6 I_3 = 40 \quad \text{--- (3)} \quad \text{By subs. (2) and (3) in (1)}$$

$$12 I_1 - 11 I_2 = -10$$

$$12 I_1 = -10 + 11 I_2$$

$$I_1 = \frac{1}{12} (-10 + 11 I_2) \Rightarrow I_1 = \frac{1}{12} (11 I_2 - 10) \quad \text{--- (4)}$$

By subs. (4) in (3)

$$11 I_2 + 6 (I_1 + I_2) = 40$$

$$11 I_2 + 6 I_1 + 6 I_2 = 40$$

$$6 I_1 + 17 I_2 = 40 \quad \text{--- (5)}$$

by subs. (4) in (5)

<<

$$6 \times \frac{1}{12} (11 I_2 - 10) + 17 I_2 = 40$$

$$5.5 I_2 - 5 + 17 I_2 = 40$$

$$22.5 I_2 = 45 \Rightarrow I_2 = \frac{45}{22.5} = 2 \text{ A}$$

From eq. (1)

$$I_1 = \frac{1}{12} \times (11 \times 2 - 10)$$

$$I_1 = \frac{1}{12} (12) \Rightarrow I_1 = 1 \text{ A}$$

$$I_3 = I_1 + I_2 = 1 + 2 = 3 \text{ A}$$


EXP.

For the following circuit find the current in each of the three resistances?

$$I_{8\Omega} = I_1$$

$$I_{15\Omega} = I_2$$

$$I_{9\Omega} = I_3$$

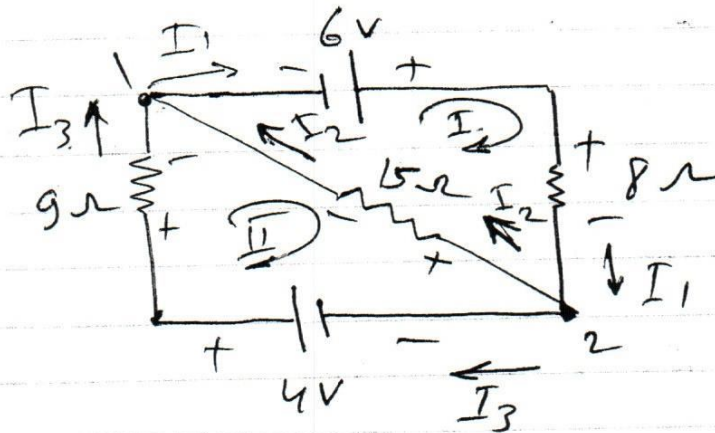

At node (1) KCL:

$$I_1 = I_2 + I_3 \Rightarrow I_3 = I_1 - I_2 \quad \text{--- (1)}$$

(18)

For Loop (I) KVL:

$$6V - 8I_1 - 15I_2 = 0$$
$$8I_1 + 15I_2 = 6 \quad \text{--- (2)}$$

$$15I_2 = 6 - 8I_1 \Rightarrow I_2 = \frac{1}{15} \times (6 - 8I_1) \quad \text{--- (3)}$$

For Loop II KVL

$$15I_2 + 4V - 9I_3 = 0$$

$$15I_2 + 4 - 9I_3 = 0 \quad \text{--- (4)}$$

by subs. (3) in (4) we obtained:

$$15I_2 + 4 - 9(I_1 - I_2) = 0$$

$$15I_2 - 9I_1 + 9I_2 + 4 = 0$$

$$24I_2 - 9I_1 + 4 = 0 \quad \text{--- (5)}$$

by subs. (3) in (5)

$$24 \times \frac{1}{15} (6 - 8I_1) - 9I_1 + 4 = 0$$

$$9.6 - 12.8I_1 - 9I_1 + 4 = 0$$

$$13.6 - 21.8I_1 = 0$$


$$21.8I_1 = 13.6 \Rightarrow I_1 = 0.6 \text{ A}$$

$$I_2 = \frac{6}{15} - \frac{8 \times 0.6}{15} = 0.4 - 0.32 = 0.08 \text{ A}$$

$$I_3 = I_1 - I_2$$
$$= 0.6 - 0.08$$
$$= 0.52 \text{ A}$$

Ex

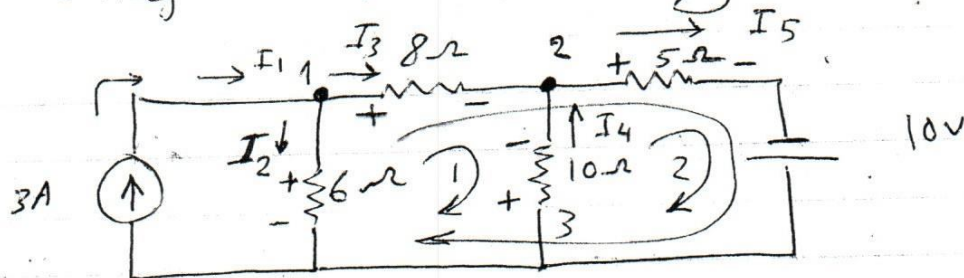Find the voltage across (8Ω) by using Kirchhoff's Law? CW



At nodes (1, 2) KCL:

$$I_1 = I_2 + I_3 \quad \text{--- (1)}$$

$$I_5 = I_3 + I_4 \quad \text{--- (2)}$$

$$I_3 = I_5 - I_4, \quad I_2 = I_1 - I_3 \Rightarrow I_2 = 3 - (I_5 - I_4) \Rightarrow$$

$$I_2 = 3 - I_5 + I_4$$

At loops (1, 2, 3) KVL:

$$6I_2 - 8I_3 + 10I_4 = 0 \quad \text{--- (3)}$$

$$-10I_4 - 5I_5 + 10 = 0$$

$$10I_4 + 5I_5 = 10 \quad \text{--- (4)}$$

$$10 + 6I_2 - 8I_3 - 5I_5 = 0$$

$$-6I_2 + 8I_3 + 5I_5 = 10 \quad \text{--- (5) By subs. } I_2 \text{ and } I_3 \text{ in (5)}$$

$$-6(3 - I_5 + I_4) + 8(I_5 - I_4) + 5I_5 = 10$$

$$-18 + 6I_5 - 6I_4 + 8I_5 - 8I_4 + 5I_5 = 10$$

$$-14I_4 + 19I_5 = 28 \quad \text{--- (6)}$$

19

Now multiply eq. (4) in 19 and eq. (6) in 5 we obtain,

$$10 I_4 + 5 I_5 = 10 \quad \text{--- (4)} \quad \times 19$$

$$-14 I_4 + 19 I_5 = 28 \quad \text{--- (6)} \quad \times 5$$

\Rightarrow

$$190 I_4 + 95 I_5 = 190$$

$$\pm 70 I_4 \mp 95 I_5 = \mp 140$$

} By
subtracting

$$260 I_4 = 50 \Rightarrow I_4 = \frac{50}{260} \approx 0.2 \text{ A}$$

from eq. (4) \Rightarrow

$$10 I_4 + 5 I_5 = 10 \Rightarrow 10 \times 0.2 + 5 I_5 = 10$$

$$2 + 5 I_5 = 10 \Rightarrow 5 I_5 = 8 \Rightarrow I_5 = \frac{8}{5} = 1.6 \text{ A}$$


$$I_3 = I_5 - I_4 = 1.6 - 0.2 = 1.4 \text{ A}$$

$$V_{8\Omega} = I_3 \times R = 1.4 \times 8 = 11.2 \text{ V}$$

$$I_2 = I_1 - I_3 = 3 - 1.4 = 1.6 \text{ A}$$

32

For the circuit shown below, find V_X .

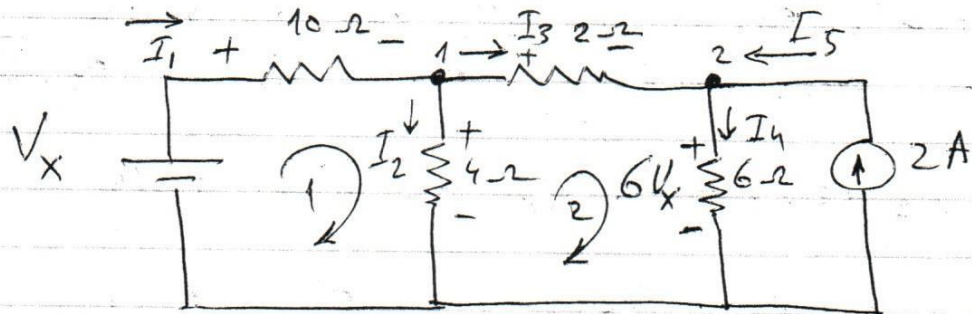

$$I_5 = 2A$$

$$I_4 = \frac{6V_X}{6} = V_X$$

$$I_5 = 2A$$

For nodes (1, 2) KCL

$$I_1 = I_2 + I_3 \quad \text{--- (1)}$$

$$I_4 = I_3 + I_5 \quad \text{--- (2)} \Rightarrow I_3 = I_4 - I_5 \Rightarrow \boxed{I_3 = V_X - 2}$$

For loops (1, 2) KVL:

$$V_X - 10I_1 - 4I_2 = 0$$

$$10I_1 + 4I_2 = V_X \quad \text{--- (3)}$$

$$4I_2 - 2I_3 - 6V_X = 0$$

$$-4I_2 + 2I_3 = -6V_X \quad \text{--- (4) By subst. (1) in (3)}$$

$$10(I_2 + I_3) + 4I_2 = V_X$$

$$10I_2 + 10I_3 + 4I_2 = V_X$$

$$14I_2 + 10I_3 = V_X \quad \text{--- (5)}$$

C0

Multiply eq. (4) in 14 and eq. (5) in -4 ~~we get~~ and subtracting eq. (5) from eq. (4) we obtain

$$-4 I_2 + 2 I_3 = -6 V_x \quad (4) \quad * 14$$

$$14 I_2 + 10 I_3 = V_x \quad (5) \quad * -4$$

$$-56 I_2 + 28 I_3 = -84 V_x \quad (4)$$

$$+ 56 I_2 + 40 I_3 = + 4 V_x \quad (5)$$

$$68 I_3 = -80 V_x \quad (6) \text{ by subst. } I_2 \text{ in (4)}$$

$$68 (V_x - 2) = -80 V_x$$

$$68 V_x - 136 = -80 V_x$$

$$68 V_x + 80 V_x = 136$$

$$148 V_x = 136 \Rightarrow V_x = \frac{136}{148} = 0.918 \text{ V} = \underline{\underline{I_4}}$$

$$I_3 = 0.918 - 2 = -1.082 \text{ A by subst. } V_x \text{ and } I_3 \text{ in (4)}$$

$$-4 I_2 + 2 * (-1.082) = -6 * (0.918) \Rightarrow$$

$$-4 I_2 - 2.164 = -5.5$$

$$I_2 = \frac{5.5}{4} = 1.375 \text{ A}$$

$$I_1 = I_2 + I_3 = 1.375 + (-1.082) = \underline{\underline{0.293 \text{ A}}}$$

Nodal Analysis

The nodal analysis depends on the First Kirchhoff's law in circuit nodes.

~~pro~~ In work method must be limit the circuit node which contain three (3) branch or more and write symbol for it voltages V_1, V_2, V_3 and consider one of these nodes as reference node ($V_{ref} = 0$), after that we must to consider currents vector at each node always out of node by using first Kirchhoff's law, and become the sum of currents equal 0


and by solve these equations we obtain on the unknowns values (V_1, V_2, \dots) and at this we can to find circuit currents.

Note:

If the voltage source (single) be between node and reference node that's mean the voltage ~~across~~ node will be known and equal value of this source.


EXP.

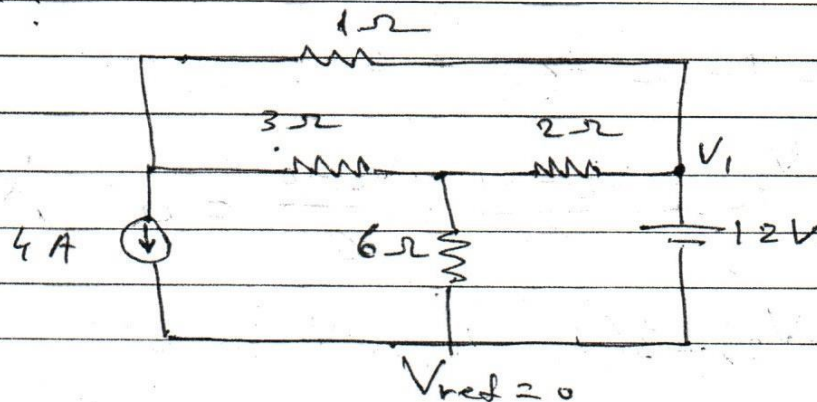Find currents of resistances for the following circuit?



Sol/

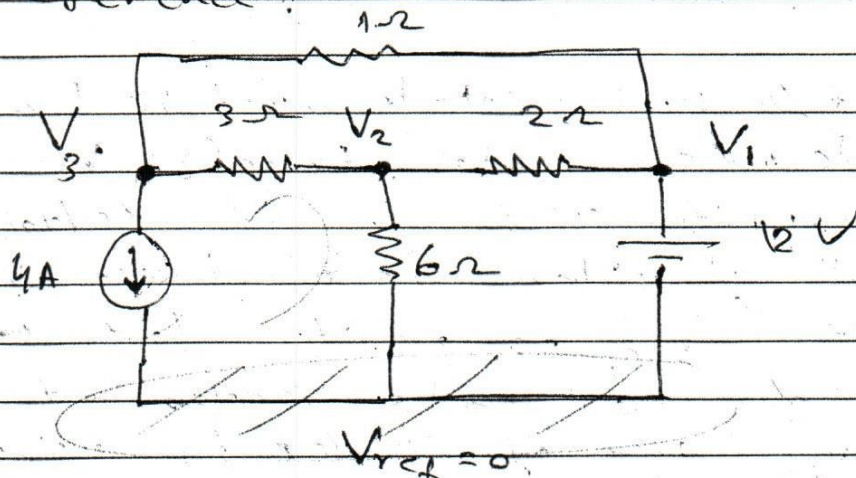
First we must to limit the circuit nodes which contains on 3 branches, and consider one of them as reference:



We see the voltage source (12V) between the node V_1 and the reference, that means the voltage node equal voltage source:

$$V_1 = 12V$$

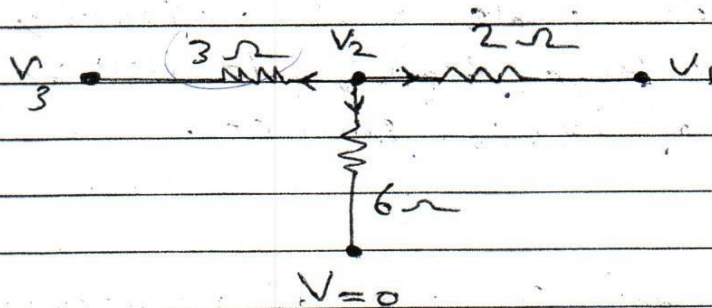Now by using first Kirchhoff's law on second node and consider all of currents out of it:



$$\sum I_{out} = 0$$

$$I_{3\Omega} + I_{2\Omega} + I_{6\Omega} = 0$$

$$\frac{V_2 - V_3}{3} + \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{6} = 0 \quad \times 6$$

$$2(V_2 - V_3) + 3(V_2 - V_1) + V_2 = 0$$


(22)

CV

$$-3V_1 + 6V_2 - 2V_3 = 0$$

$$-3 \times 12 + 6V_2 - 2V_3 = 0$$
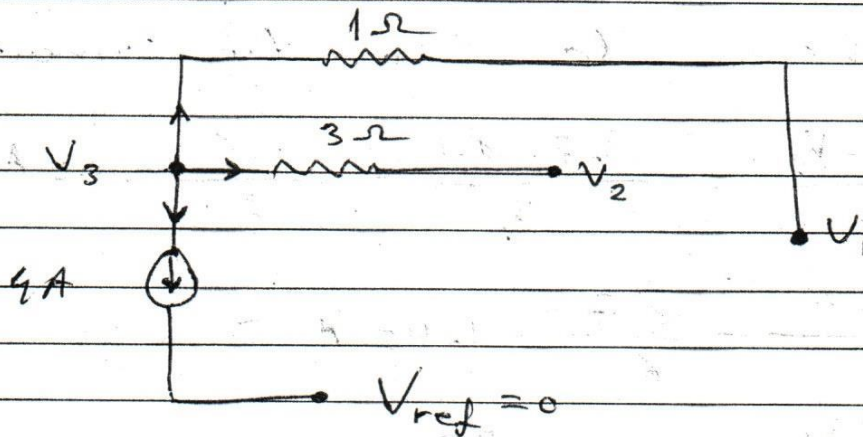
$$6V_2 - 2V_3 = 36 \quad \text{--- (1)} \quad \times 4$$



$$\sum I_{out} = 0$$

$$I_{1\Omega} + I_{3\Omega} + 4 = 0$$

$$\frac{V_3 - V_1}{1} + \frac{V_3 - V_2}{3} + 4 = 0 \quad \times 3$$

$$3(V_3 - V_1) + V_3 - V_2 + 12 = 0$$

$$-3V_1 - V_2 + 4V_3 + 12 = 0$$

$$(-3 \times 12) - V_2 + 4V_3 + 12 = 0$$

$$-V_2 + 4V_3 = 24 \quad \text{--- (2)} \quad \times 2$$

$$24V_2 - 8V_3 = 144 \quad \text{--- (1)}$$

$$-2V_2 + 8V_3 = 48 \quad \text{--- (2)}$$

+

$$22V_2 = 192$$

 \Rightarrow

$$V_2 = \frac{192}{22} = 8.7V$$

$$6 \times 8.7 - 2V_3 = 36$$

$$52.2 - 36 = 2V_3$$

$$16.2 = 2V_3 \Rightarrow V_3 = \frac{16.2}{2} = 8.1 \text{ V}$$

At least we can find the currents,

$$I_{3\Omega} = \frac{V_2 - V_3}{3} = \frac{8.7 - 8.1}{3} = \frac{0.6}{3} = 0.2 \text{ A}$$

$$I_{6\Omega} = \frac{V_2 - 0}{6} = \frac{8.7}{6} = 1.45 \text{ A}$$

$$I_{2\Omega} = \frac{V_1 - V_2}{2} = \frac{12 - 8.7}{2} = \frac{3.3}{2} = 1.65 \text{ A}$$


$$I_{1\Omega} = \frac{V_1 - V_3}{1} = \frac{12 - 8.1}{1} = 3.8 \text{ A}$$

we must calculate the source current (12V) which can calculate from first node:

$$I_s = I_{2\Omega} + I_{1\Omega}$$

$$= 1.65 + 3.8$$


$$= 5.45 \text{ A}$$

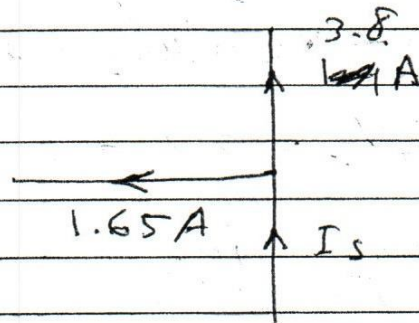


EXP.

CA

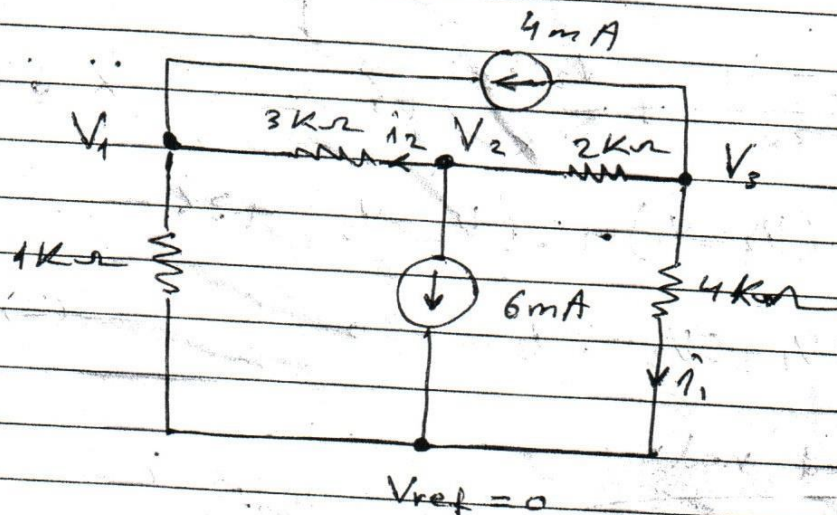Find i_1, i_2 for the following circuit by using nodal analysis?



Sol

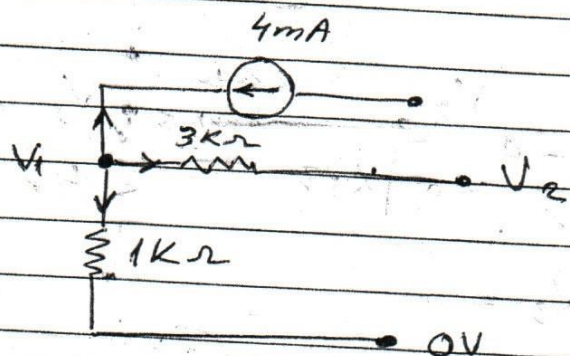

First node:


$$\sum I_{out} = 0$$

$$\left(4mA + \frac{V_1 - V_2}{3k} + \frac{V_1 - 0}{1k} = 0 \right) \times 3k$$

$$-12 + V_1 - V_2 + 3V_1 = 0$$

$$4V_1 - V_2 = 12 \quad (1)$$

Second node:

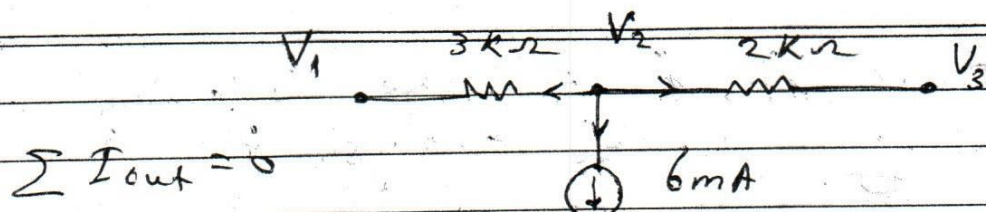


$$\sum I_{out} = 0$$

$$\left(\frac{V_2 - V_1}{3K} + \frac{V_2 - V_3}{2K} + 6m \right) \times 6K = 0$$

$$2(V_2 - V_1) + 3(V_2 - V_3) + 36 = 0$$

$$-2V_1 + 5V_2 - 3V_3 = -36 \quad (2)$$

● Third node

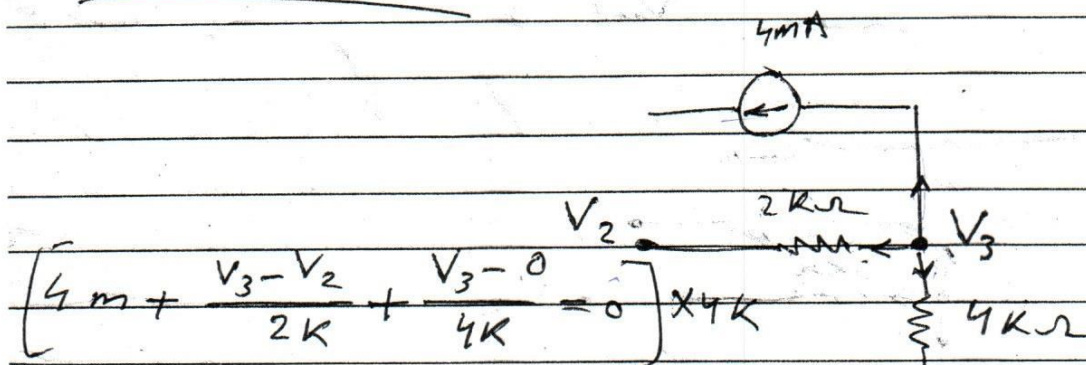

$$\left[4m + \frac{V_3 - V_2}{2K} + \frac{V_3 - 0}{4K} \right] \times 4K = 0$$

$$16 + 2(V_3 - V_2) + V_3 = 0$$

$$-2V_2 + 3V_3 = -16 \quad (3)$$

From Eq. (1)

$$4V_1 - V_2 = 12 \Rightarrow 4V_1 = 12 - V_2$$

$$V_1 = 3 - \frac{V_2}{4} \quad (4)$$

by Subst. (4) in (2)

$$-6 + \frac{V_2}{2} + 5V_2 - 3V_3 = -36$$

$$\frac{V_2 + 10V_2}{2} - 3V_3 = -30 \quad \times 2$$

(24)

C9

$$11V_2 - 6V_3 = -90 \quad \text{--- (5) } / \times 2$$

$$-2V_2 + 3V_3 = -16 \quad \text{--- (3) } / \times 11$$

$$22V_2 - 12V_3 = -180$$

$$-22V_2 + 33V_3 = -176$$

$$21V_3 = -356$$

$$V_3 = -16.9 \text{ V}$$

From eq. (5)

$$11V_2 + 6 \times -16.9 = -90$$

$$11V_2 = -191.4 \Rightarrow V_2 = -17.4 \text{ V}$$

From eq. (4)


$$V_1 = 3 - \frac{V_2}{4} = 3 - \frac{17.4}{4} = 3 - 4.35 = -1.35 \text{ V}$$

$$i_2 = \frac{V_2 - V_1}{3 \text{ K}} = \frac{-17.4 - (-1.35)}{3 \text{ K}} = \frac{-16.05}{3 \text{ K}} = -5.35 \text{ mA}$$

$$i_1 = \frac{V_3 - 0}{4 \text{ K}} = \frac{-16.9}{4} = -4.225 \text{ mA}$$

Exp

Find I_x by using nodal analysis?

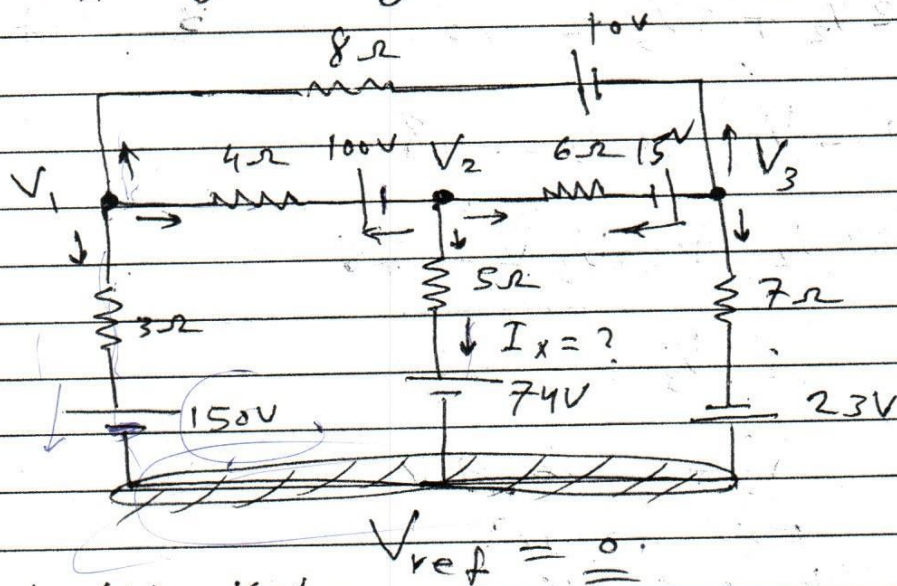

Sol AT node (1) KCL;

$$\frac{V_1 - 0 - 150}{3} + \frac{V_1 - V_2 - 100}{4} + \frac{V_1 - V_3 - 10}{8} = 0 \quad \times 24$$

$$8V_1 - 1200 + 6V_1 - 6V_2 - 600 + 3V_1 - 3V_3 - 30 = 0$$

$$17V_1 - 6V_2 - 3V_3 = 1830 \quad \text{--- (1)} \quad \times 20 \quad / \quad \times 146$$

AT node (2):

$$\frac{V_2 - V_1 + 100}{4} + \frac{V_2 - 0 - 74}{5} + \frac{V_2 - V_3 + 15}{6} = 0 \quad \times 120$$

$$30V_2 - 30V_1 + 300 + 24V_2 - 1776 + 20V_2 - 20V_3 + 300 =$$

$$-30V_1 + 74V_2 + 20V_3 = 1176 \quad \text{--- (2)} \quad \times -3$$

$$\text{AT node (3): } \frac{V_3 - V_1 + 10}{8} + \frac{V_3 - V_2 - 15}{6} + \frac{V_3 - 0 + 23}{7} = 0 \quad \times 336$$

$$42V_3 - 42V_1 + 420 + 56V_3 - 56V_2 - 840 + 48V_3 + 1104 = 0$$

$$-42V_1 - 56V_2 + 146V_3 = -684 \quad \text{--- (3)} \quad \times -3$$

(25)

w.

$$340V_1 - 120V_2 - 60V_3 = 36600 \quad (1)$$

$$+90V_1 + 222V_2 + 60V_3 = +3528 \quad (2)$$

$$250V_1 + 102V_2 = 40128 \quad (4) \quad \text{by subtraction}$$

$$2482V_1 - 876V_2 - 438V_3 = 267180 \quad (1)$$

$$+126V_1 + 168V_2 + 438V_3 = +2052 \quad (3)$$

by subs.

$$2356V_1 - 1044V_2 = 265128 \quad (5) \quad \times 102$$

$$261000V_1 - 106488V_2 = -41893632 \quad (4)$$

$$+240312V_1 + 106488V_2 = +27043056 \quad (5)$$

subtraction

$$501312V_1 = 68936688$$

$$V_1 = \frac{68936688}{501312} = 137.5 \quad V \quad \text{by subst. in (4)}$$

$$250 \times 137.5 + 102V_2 = 40128$$

$$102V_2 = 40128 - 34375 = 5753$$

$$102V_2 = 5749.8 \Rightarrow V_2 = \frac{5749.8}{102} = 56.37 \quad V$$

By subs. V_1 and V_2 in (1)

$$17 \times 137.5 - 6 \times 56.37 - 3V_3 = 1830$$

$$2337.5 - 338.22 - 3V_3 = 1830$$

$$1999.28 - 3V_3 = 1830$$

$$1999.28 - 1830 = 3V_3$$


$$9.28 = 3V_3 \Rightarrow V_3 = \frac{169.28}{3} = 56.4 \text{ V}$$

$$I_X = \frac{V_2 - V_{\text{ref}} - 74}{5} = \frac{56.37 - 74}{5} = \frac{-17.63}{5}$$

$$I_X = -3.526 \text{ A}$$

Exp.

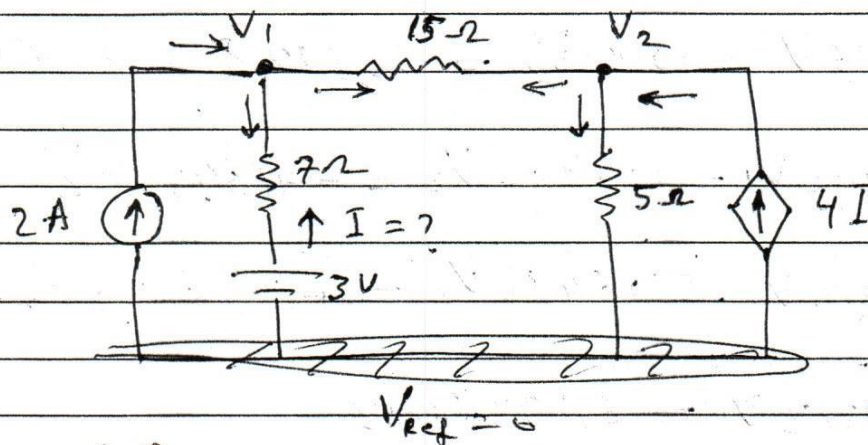For the circuit below, calculate the value of (I) using noded analysis?



Sol At node ①

$$\frac{V_1 - V_2}{15} + \frac{V_1 - 0 - 3}{7} = 2$$

$$\frac{V_1 - V_2}{15} + \frac{V_1 - 3}{7} = 2 \quad * 105$$

$$7V_1 - 7V_2 + 15V_1 - 45 = 210$$

$$22V_1 - 7V_2 = 255 \quad \text{--- (1)} \quad * 20$$

$$I = - \left(\frac{V_1 - 0 - 3}{7} \right)$$

$$\boxed{I = \frac{3 - V_1}{7}}$$

At node: ②

$$\frac{V_2 - V_1}{15} + \frac{V_2 - 0}{5} = 4I \quad * 75$$

$$-5V_1 + 20V_2 = 300I \quad \text{by sub. I in it.}$$

$$-5V_1 + 20V_2 = 300 \times \frac{3 - V_1}{7}$$

$$-5V_1 + 20V_2 = 128.5 - 42.8V_1$$

$$+42.8V_1 - 5V_1 + 20V_2 = 128.5$$

$$37.8V_1 + 20V_2 = 128.5 \quad \text{②} \quad * -7$$

$$440V_1 - 140V_2 = 5100 \quad \text{①}$$

$$+264.6V_1 + 140V_2 = +899.5 \quad \text{②}$$

by subtracting

$$704.6V_1 = 5999.5$$

$$V_1 = \frac{5999.5}{704.6} = 8.5V \quad \text{by sub. in ①}$$

$$22 \times 8.5 - 7 \times V_2 = 255$$

$$187.3 - 7V_2 = 255$$

$$-7V_2 = 255 - 187.3$$

$$-7V_2 = 67.6$$


$$V_2 = \frac{-67.6}{7} = -9.6V$$

$$I = \frac{3 - V_1}{7} = \frac{3 - 8.5}{7} = \frac{-5.5}{7}$$

$$= -0.785A$$

EXP.

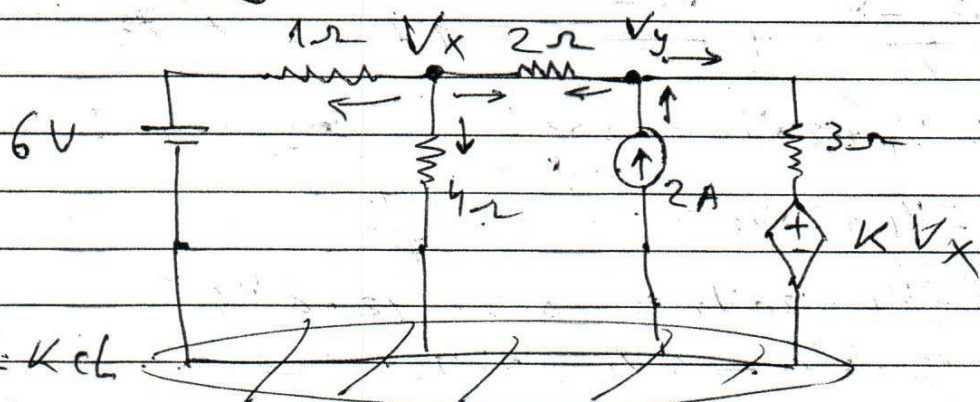Find the value of (K) which makes $(V_y = 0)$ by using node analysis?



At node X: KCL

$$\frac{V_x - 0 - 6}{1} + \frac{V_x - 0}{4} + \frac{V_x - V_y}{2} = 0 \quad V_{ref} = 0$$

$$\frac{V_x - 6}{1} + \frac{V_x}{4} + \frac{V_x - V_y}{2} = 0 \quad (1)$$

When $V_y = 0$

$$V_x - 6 + \frac{V_x}{4} + \frac{V_x - 0}{2} = 0 \quad * 4$$

$$4V_x - 24 + V_x + 2V_x = 0 \quad \therefore 7V_x - 24 = 0$$

$$V_x = \frac{24}{7} = 3.4 \text{ V}$$

At node Y:

$$\frac{V_y - V_x}{2} + \frac{V_y - 0 - KV_x}{3} = 2 \Rightarrow \frac{V_y - V_x}{2} + \frac{V_y - KV_x}{3} = 2$$

$$3V_x - 2KV_x = 12 \Rightarrow -3 \times 3.4 - 2 \times 3.4K = 12$$

$$-10.2 - 6.8K = 12$$

$$-6.8K = 12 + 10.2$$

$$-6.8K = 22.2 \Rightarrow K = \frac{-22.2}{6.8} = \underline{\underline{-3.2}}$$

(27)

حل المسألة

MAXwell Analysis is Mesh current Loop analysis

By Solving this method we must use

The Kirchhoffs Voltage law but by using
Loops current.

Steps of solution:


1. Limit number of closed loop.
2. The number of equations = equal number of loop.
3. consider for each loop its current and its vector with clock wise.
4. The current between two loop to solve this case we must use (Super mesh).

In case Super mesh:

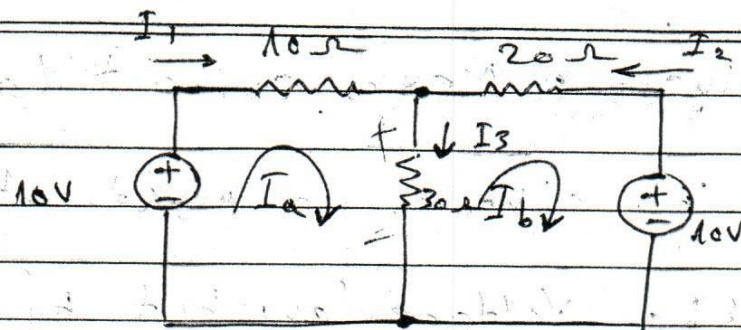1. we take the due of source.
2. eliminate the source and put in his place open circuit.
3. Consider the current equation for the open loop as a one loop.

Exp

Calculate the currents for the following circuit by using currents loop (Maxwell analysis)



Soln //

loop a

$$10V - 10\Omega I_1 + 30\Omega I_a + 30\Omega I_b = 0 \quad \text{--- (1)}$$

$$-40I_a + 30I_b = -10$$

$$-40I_a + 30I_b = -10 \quad / \text{ by dividing by } 10$$

$$-4I_a + 3I_b = -1 \quad \text{--- (1)} \quad / \times 5$$

loop b

$$-10 + 30I_a - 30I_b - 20I_b = 0$$

$$30I_a - 50I_b = 10 \quad / \div 10$$

$$3I_a + 5I_b = -1 \quad \text{--- (2)} \quad / \times 3$$

$$-20I_a + 15I_b = -5 \quad \text{--- (1)}$$

by sub. $9I_a + 15I_b = -3 \quad \text{--- (2)}$

by add. $11I_a = -2 \Rightarrow I_a = \frac{-2}{11} = -0.1818 \text{ A}$

From eq. (2) find the I_b !

$$-3 \times -0.181 + 5I_b = -1$$

$$0.181 + 5I_b = -1$$

$$5I_b = -1.181 \quad \text{--- (1)}$$

$$I_b = \frac{-1.181}{5} = -0.236 \text{ A}$$

$$I_a = I_1 = \cancel{0.181 A} = 0.181 A$$


$$I_b = -I_2 = -(\cancel{0.6309}) = \cancel{0.091 A} = 0.309 A$$

$$I_3 = I_a - I_b = 0.181 - 0.091 = 0.272 A$$

$$= \cancel{0.181} - \cancel{0.636} = \cancel{1.363 A}$$

$$\underline{\text{Exp.}} \quad -0.181 - 0.309 = -0.49 A$$

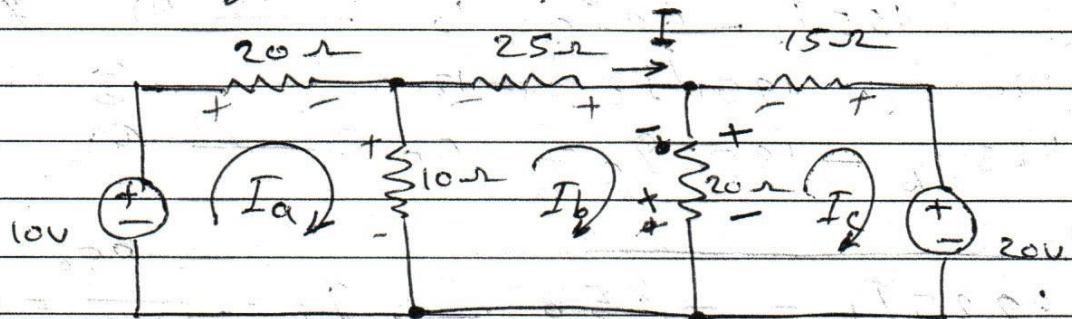calculate the loop currents for the following circuit?



Sol

Loop a

$$10 - 20I_a - (I_a - I_b)10 = 0$$

$$-20I_a - 10I_a + 10I_b = -10$$

$$-30I_a + 10I_b = -10 \quad / \div -10$$

$$3I_a - I_b = 1 \quad \text{--- (1) } \times 10$$

Loop b

$$10(I_b - I_a) + 25I_b + 20(I_b - I_c) = 0$$

$$10I_b - 10I_a + 25I_b + 20I_b - 20I_c = 0$$

$$-10I_a + 55I_b - 20I_c = 0 \quad \text{--- (2) } \times 3$$

⑤

4/3

$$20(I_c - I_b) + 15I_c = -20 \quad (1)$$

$$20I_c - 20I_b + 15I_c = -20$$

$$-20I_b + 35I_c = -20 \quad (3) \quad \times 60$$

$$30I_a - 10I_b = 10 \quad (4)$$

$$-30I_a + 165I_b - 60I_c = 0 \quad (2)$$

by add.

$$155I_b - 60I_c = 10 \quad (4) \quad \times 35$$

$$= 1200I_b + 1950I_c = -1200 \quad (3)$$

$$5425I_b - 1950I_c = 350 \quad (4)$$

by add.

$$4225I_b = -850 \Rightarrow I_b = \frac{-850}{4225} = -0.201 \text{ A}$$

from eq (3) we can find $I_c =$

$$= 20 \times -0.201 + 35I_c = -20$$

$$35I_c = -24.02 \Rightarrow I_c = \frac{-24.02}{35} = -0.686 \text{ A}$$

from eq (1) we can find $I_a =$


$$3I_a - (-0.201) = 1$$

$$3I_a = 1 - 0.201 = 0.799 \Rightarrow I_a = \frac{0.799}{3} = 0.266 \text{ A}$$

$$I_a = 0.266 \text{ A}$$


$$I_b = -0.201 \text{ A}$$

$$I_c = -0.686 \text{ A}$$

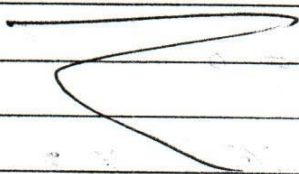

EXP.

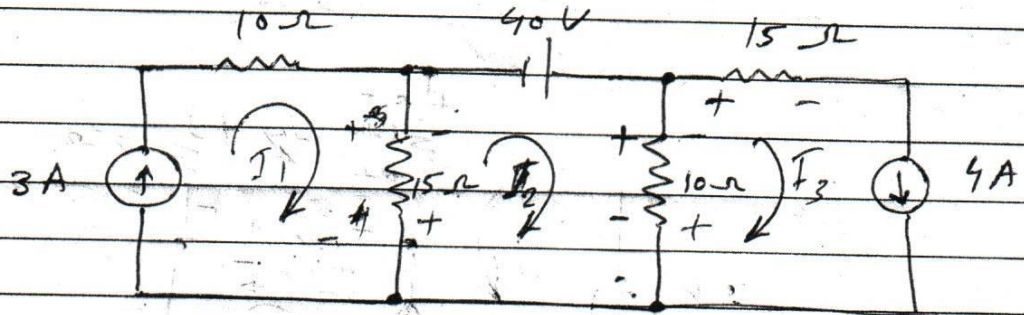Find the power in 40V by using Maxwell Analysis (Mesh current loop analysis)



AT Loop ① KVL:

$$I_1 = 3A$$

AT Loop ② KVL

$$40 - 10(I_2 - I_3) - 15(I_2 - I_1) = 0$$

$$40 - 10I_2 + 10I_3 - 15I_2 + 15I_1 = 0$$

$$15I_1 - 25I_2 + 10I_3 = -40$$

$$-25I_2 + 10I_3 = -85$$

$$25I_2 - 10I_3 = 85 \quad \text{--- (1)}$$

AT loop (3) KVL:

$$I_3 = 4A$$

$$25I_2 - 10 \times 4 = 85$$


$$25I_2 = 85 + 40 \Rightarrow 25I_2 = 125$$

$$I_2 = \frac{125}{25} = 5A$$

$$\begin{aligned} \text{power in } 40V &= V \times I_2 \\ &= 40 \times 5 = 200W \end{aligned}$$

EXP

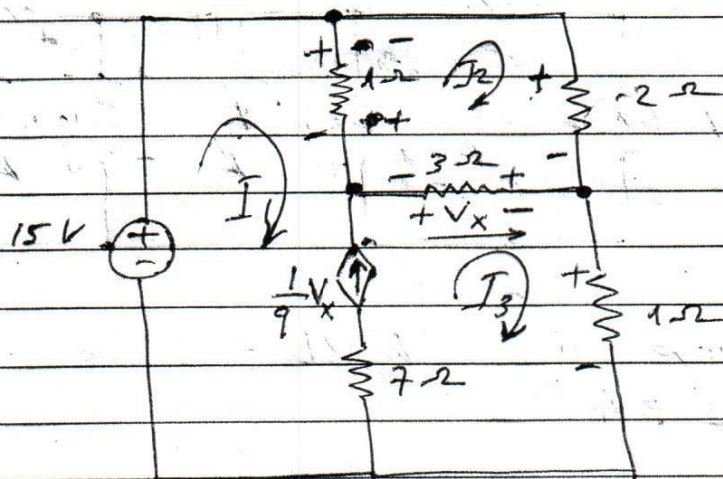Find I_1, I_2, I_3 by using mesh analysis then find V_x ?



Sol

$$I_3 - I_1 = \frac{1}{9} V_x \quad \text{--- (1)}$$

AT super mesh (make current source as open circuit)

$$+15 - 1 \times (I_1 - I_2) - 3(I_3 - I_2) - 1I_3 = 0$$

$$15 - I_1 + I_2 - 3I_3 + 3I_2 - I_3 = 0$$

$$-I_1 + 4I_2 - 4I_3 = -15$$

$$I_1 - 4I_2 + 4I_3 = 15 \quad \text{--- (2) } \times 2$$


AT Loop (2) KVL:

$$-1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0$$

$$I_1 - I_2 - 2I_2 - 3I_2 + 3I_3 = 0$$

$$I_1 - 6I_2 + 3I_3 = 0$$
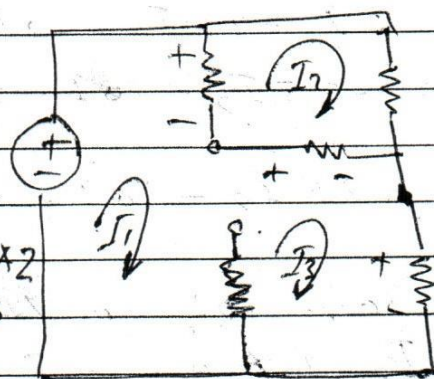
$$-I_1 + 6I_2 - 3I_3 = 0 \quad \text{--- (3) } \times 4$$



from eq. ①

$$I_3 - I_1 = \frac{1}{9} \times \underbrace{3(I_3 - I_2)}_{V_x} \times 3$$

$$3I_3 - 3I_1 = I_3 - I_2$$

$$3I_3 - 3I_1 - I_3 + I_2 = 0$$

$$-3I_1 + I_2 + 2I_3 = 0 \quad \text{--- (4)} \quad \times 4$$

$$2I_1 - 8I_2 + 8I_3 = 30 \quad \text{--- (2)}$$

$$+12I_1 + 4I_2 + 8I_3 = 0 \quad \text{--- (4)}$$

$$\text{by sub.} \\ 14I_1 - 12I_2 = 30 \quad \text{--- (5)}$$

eq ② and ③

$$-3I_1 + 12I_2 - 12I_3 = -45 \quad \text{--- (2)}$$

$$+4I_1 + 24I_2 + 12I_3 = 0 \quad \text{--- (3)}$$

by sub.

$$I_1 - 12I_2 = -45 \quad \text{--- (6)}$$

$$I_1 = -45 + 12I_2 \quad \text{substitute in eq. (5)}$$

$$14 \times -45 + 14 \times 12I_2 - 12I_2 = 30$$

$$-630 + 156I_2 = 30$$

$$I_2 = \frac{660}{156} = 4.23 \text{ A}$$

$$= I_1 = -45 + 12 \times 4.23$$

$$= 5.77 \text{ A}$$

From eq. (4) we can find I_3 :


$$-3 \times 5.77 + 4.23 = -2 I_3$$

$$-2 I_3 = -13.08 \Rightarrow I_3 = 6.5 \text{ A}$$

$$V_x = 3 \times (I_3 - I_2) = 3 \times (6.5 - 4.23)$$

$$V_x = 6.81 \text{ V}$$

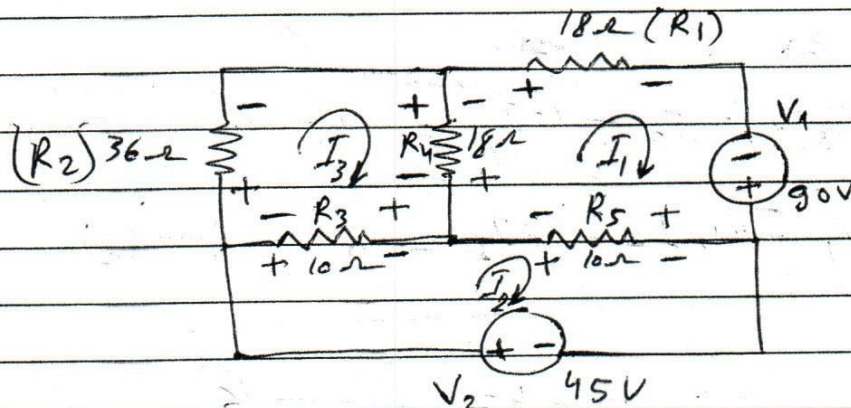EXP. In the following circuit, find the current in the branch of mesh by using Maxwell analysis or (loop current analysis)?



Sol

Loop I_1 :

$$-18 I_1 + 90 - 10(I_1 - I_2) - 18(I_1 - I_3) = 0$$

$$-18 I_1 - 10 I_1 + 10 I_2 - 18 I_1 + 18 I_3 = -90$$

$$-46 I_1 + 10 I_2 + 18 I_3 = -90$$

$$46 I_1 - 10 I_2 - 18 I_3 = 90 \quad \text{--- (1) } \times 10 / \times 46$$

31

Loop I_2 :

$$45 - 10(I_2 - I_3) - 10(I_2 - I_1) = 0$$

$$-10I_2 + 10I_3 - 10I_2 + 10I_1 = -45$$

$$10I_1 - 20I_2 + 10I_3 = -45$$

$$-10I_1 + 20I_2 - 10I_3 = 45 \quad \text{--- (2) } \times 18$$

Loop I_3 :

$$-36I_3 - 18(I_3 - I_1) - 10(I_3 - I_2) = 0$$

$$-36I_3 - 18I_3 + 18I_1 - 10I_3 + 10I_2 = 0$$

$$18I_1 + 10I_2 - 64I_3 = 0$$

$$-18I_1 - 10I_2 + 64I_3 = 0 \quad \text{--- (3) } / \times 18$$

$$460I_1 - 100I_2 - 180I_3 = 900 \quad \text{--- (1)}$$

$$+180I_1 + 360I_2 + 180I_3 = +810 \quad \text{--- (2)}$$

$$640I_1 - 460I_2 = 90 \quad \text{--- (4) } \text{By sub.} / \times 820$$

$$2944I_1 - 640I_2 - 1152I_3 = 5760 \quad \text{--- (1)}$$

$$-324I_1 - 180I_2 + 1152I_3 = 0 \quad \text{--- (3)}$$

$$2620I_1 - 820I_2 = 5760 \quad \text{--- (5) } \text{By add.} / \times 460$$

$$524800I_1 - 377200I_2 = 73800 \quad \text{--- (4)}$$

$$+1205200I_1 + 377200I_2 = +2649600 \quad \text{--- (5)}$$

$$-680400I_1 = -2575800 \quad \text{by sub}$$

$$I_1 = 3.785 \text{ A}$$

37

From eq. (4) we can find I_2 :

$$640 \times 3.785 - 460 I_2 = 90$$

$$2422.4 - 90 = 460 I_2 \Rightarrow$$

$$I_2 = 5.07 \text{ A}$$

From eq. (4) we can find I_3 :

$$46 \times 3.785 - 10 \times 5.07 - 18 I_3 = 90$$

$$174.11 - 50.7 - 90 = 18 I_3$$

$$33.41 = 18 I_3 \Rightarrow I_3 = 1.856 \text{ A}$$

$$\therefore I_{R1} = I_1 = 3.785 \text{ A}$$

$$I_{R2} = I_3 = 1.856 \text{ A}$$


$$I_{R4} = I_1 - I_3 = 3.785 - 1.856 = 1.929 \text{ A}$$

$$I_{R3} = I_2 - I_3 = 5.07 - 1.856 = 3.214 \text{ A}$$

$$I_{R5} = I_2 - I_1 = 5.07 - 3.785 = 1.285 \text{ A}$$

EXE

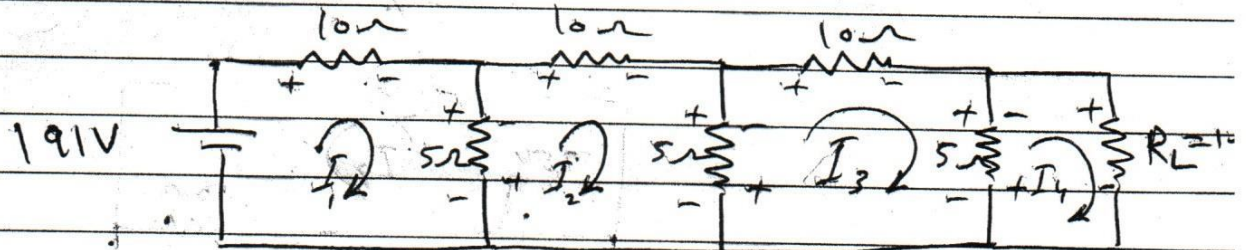Find the power of $R_L = 1\Omega$ using mesh current (loop current)?



AT Loop (1) KVL:

$$19 - 10I_1 - 5(I_1 - I_2) = 0$$

$$-10I_1 - 5I_1 + 5I_2 = -19$$

$$15I_1 - 5I_2 = 19 \quad \text{--- (1)}$$

AT Loop (2) KVL:

$$-5I_2 + 5I_1 - 10I_2 - 5I_2 + 5I_3 = 0$$

$$5I_1 - 20I_2 + 5I_3 = 0$$

$$-5I_1 + 20I_2 - 5I_3 = 0 \quad \text{--- (2)}$$

AT Loop (3) KVL:

$$-5I_3 + 5I_2 - 10I_3 - 5I_3 + 5I_4 = 0$$

$$5I_2 - 20I_3 + 5I_4 = 0$$

$$-5I_2 + 20I_3 - 5I_4 = 0 \quad \text{--- (3)}$$

AT Loop (4) KVL:

$$-5I_4 + 5I_3 - 1I_4 = 0$$

$$5I_3 - 6I_4 = 0$$


$$-5I_3 + 6I_4 = 0 \quad \text{--- (4)}$$

By adding (1) and (4), the result subtract from (3)

$$I_4 = ? \Rightarrow P_{1\Omega} = I_4^2 * R$$

EXP.

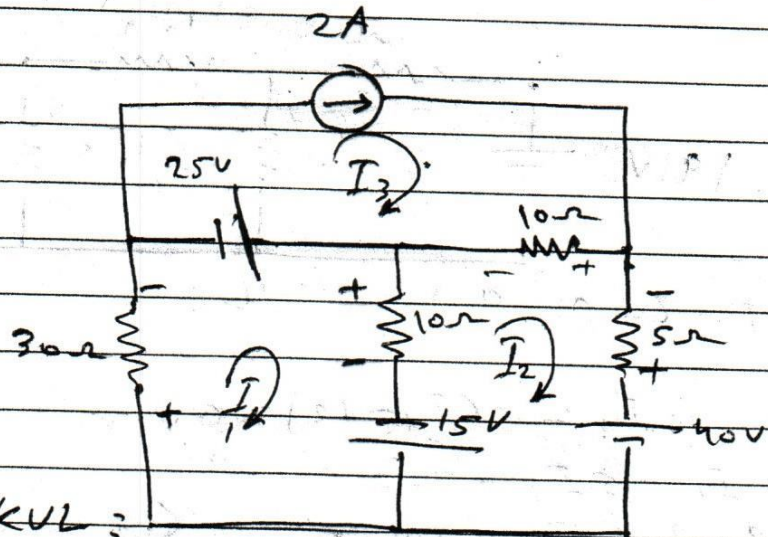Find the current for circuit shown below by using mesh analysis or Maxwell analysis



AT Loop (3) KVL:

$$I_3 = 2A \quad \text{--- (1)}$$

AT Loop (1) KVL:

$$-30I_1 + 25 - 10I_1 + 10I_2 + 15 = 0$$

$$-30I_1 - 10I_1 + 10I_2 + 40 = 0$$

$$-40I_1 + 10I_2 = -40$$

$$40I_1 - 10I_2 = 40 \quad \text{--- (2)}$$

AT Loop (2) KVL:

$$-15 + 10I_2 - 10I_1 + 10I_2 - 10I_3 + 5I_2 - 40 = 0$$

$$-10I_1 + 25I_2 - 10I_3 = 55$$

$$-10I_1 + 25I_2 = 55 + 10 \times 2$$

$$-10I_1 + 25I_2 = 75 \quad \text{--- (3)}$$

by subtract eq (3) from (2) we can find I_1

$$I_1 = (\quad) A$$

$$I_2 = (\quad) A$$

Superposition Theorem


The ST used for Analysing electric circuits which contain more of voltage sources & current sources.

Notes:


- The current sources compensate by open circuit.
- The voltage sources compensate by short circuits.

Statement & Solution steps

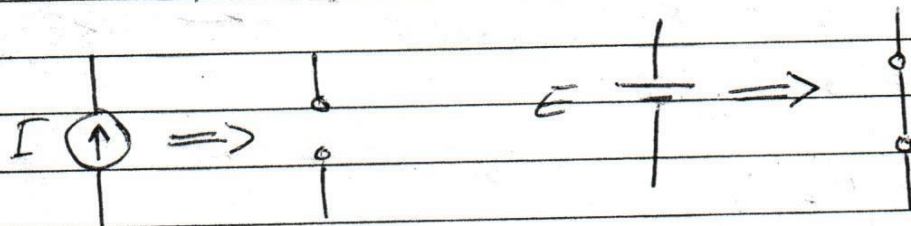- 1- We take only one source.
- 2- Find the current or voltage for each source.
- 3- Add these currents or voltages.



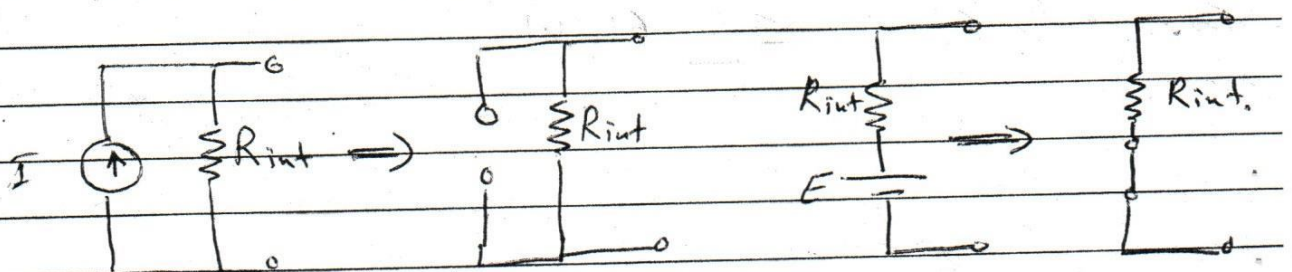
In case the voltage or current source has internal resistance we will get this:



exp.


Find the power in 1Ω by using superposition

$$P_{1\Omega} = \bar{I}_1^2 \times R$$

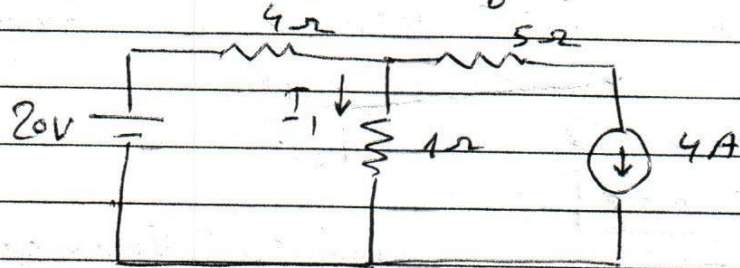

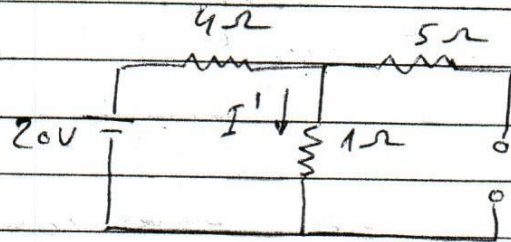1. effect 20V:


$$I' = \frac{20}{4+1} = \frac{20}{5} = 4A$$



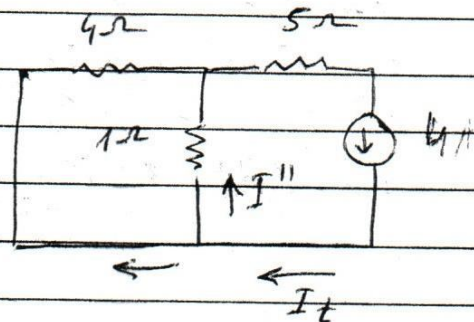2. effect 4A:

$$I'' = I_t \times \frac{4}{4+1}$$

$$I'' = 4 \times \frac{4}{5} = \frac{16}{5} = 3.2A$$



$$I_1 = 4 - 3.2 = 0.8A$$

$$P_{1\Omega} = \bar{I}_1^2 \times R$$

$$P_{1\Omega} = (0.8)^2 \times 1 = 0.64W$$

exp.


For the circuit find I using superposition theorem?

1- effect 20V;

$$R_{eq} = 10 \parallel 30 = 7.5 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{20}{7.5}$$


$$= 2.666 \text{ A}$$

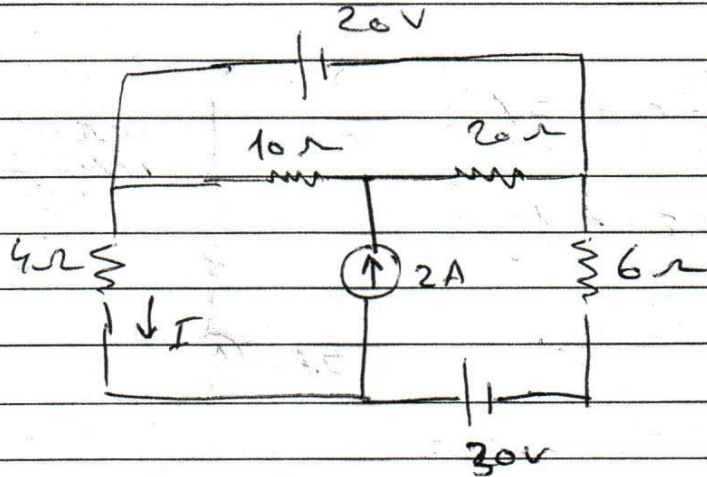

$$I' = 2.666 \times \frac{30}{40} = 2 \text{ A}$$


2- effect 30V:

$$I'' = \frac{30}{10} = 3 \text{ A}$$

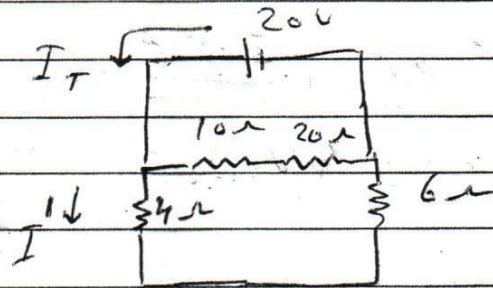

3- effect 2A:

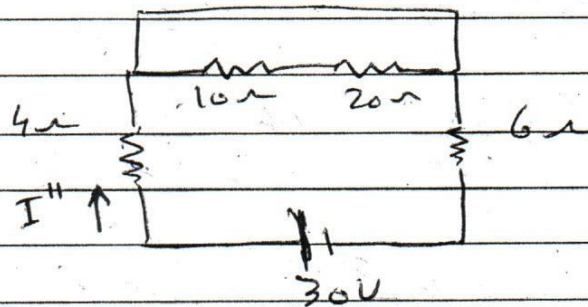
$$I''' = 2 \times \frac{6}{10} = 1.2 \text{ A}$$



$$I = I' - I'' + I'''$$

$$= 2 - 3 + 1.2$$

$$= 0.2 \text{ A}$$

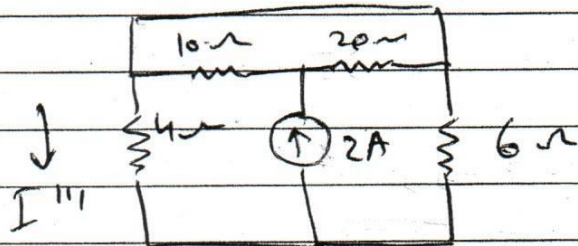

exp.

Find the current I in this figure by using Superposition?

1- effect 7A :

$$20 \parallel 20 = 10 \Omega$$

$$10 + 5 = 15 \Omega$$

$$15 \parallel 15 = 7.5 \Omega$$

$$I' = 7 \times \frac{15}{30} = \underline{\underline{3.5 A}}$$

2- effect 10V :

$$I'' = \frac{10}{30} = \underline{\underline{0.33 A}}$$





3- effect 30V :

$$I_T = \frac{30}{30} = 1 A$$

$$I''' = 1 \times \frac{20}{40} = \underline{\underline{0.5 A}}$$

$$I = 3.5 + 0.33 - 0.5$$

$$= \underline{\underline{3.33 A}}$$

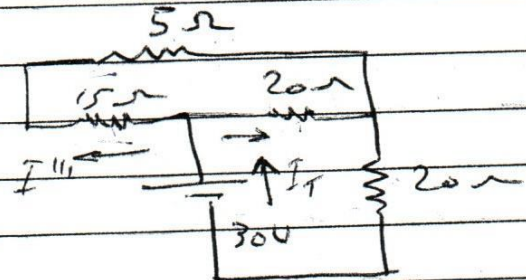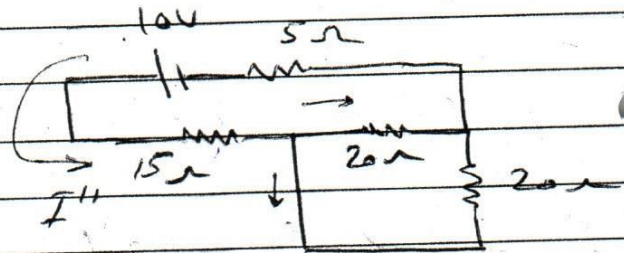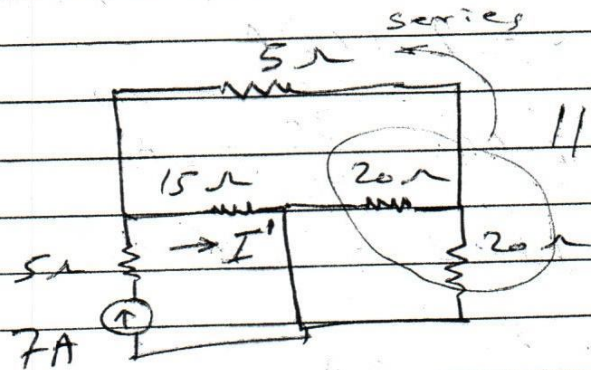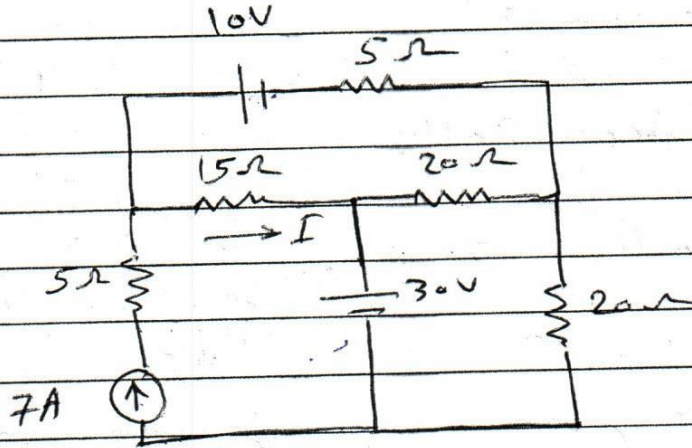


EXP. For the circuit shown below, find V_x using superposition theorem?

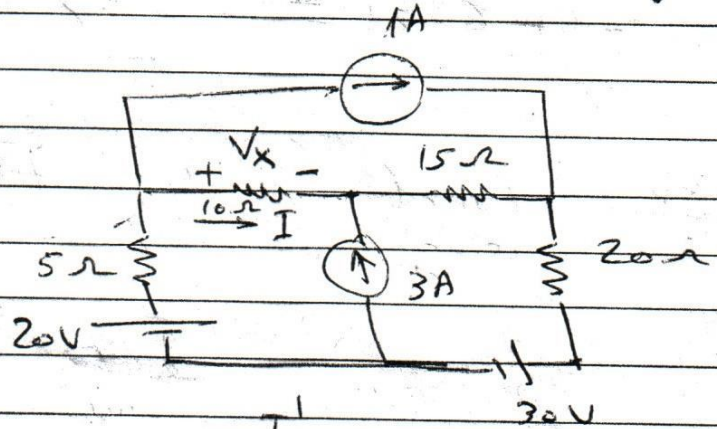1. effect 20V

$$I' = \frac{20}{50} = 0.4 \text{ A}$$


$$V_{x1} = 0.4 \times 10 = 4 \text{ V (+)}$$



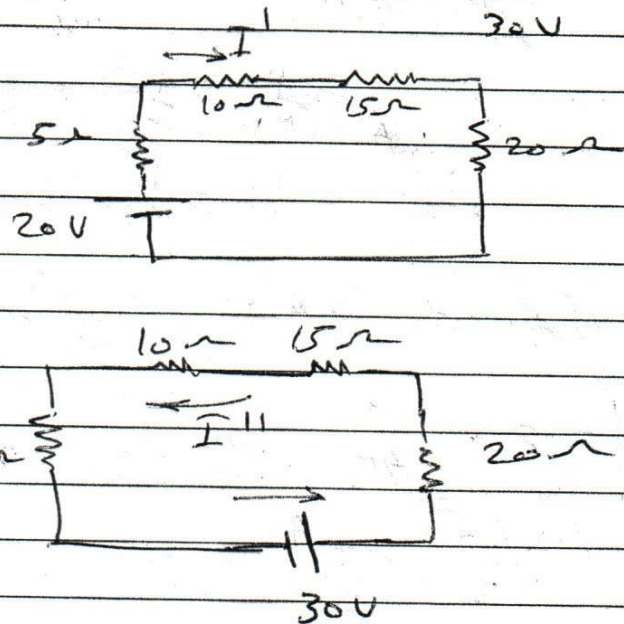2. effect 30V:

$$I'' = \frac{30}{50} = 0.6 \text{ A}$$


$$V_{x2} = 0.6 \times 10 = 6 \text{ V (-)}$$



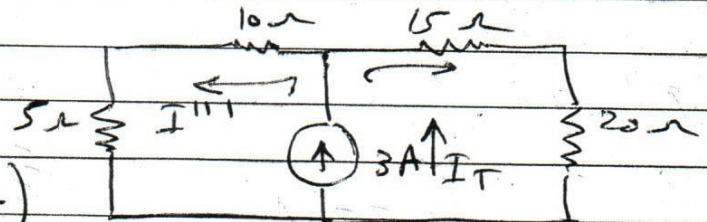3. effect 3A:

$$I''' = 3 \times \frac{35}{50} = 2.1 \text{ A}$$


$$V_{x3} = 2.1 \times 10 = 21 \text{ V (-)}$$



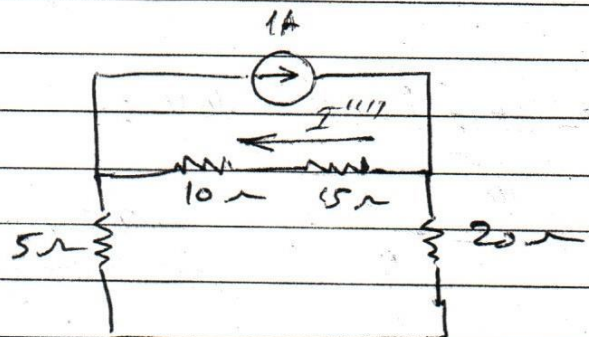4. effect 1A:

$$I'''' = 1 \times \frac{25}{50} = 0.5 \text{ A}$$


$$V_{x4} = 0.5 \times 10 = 5 \text{ V (-)}$$



$$V_{XT} = V_{X1} + V_{X2} + V_{X3} + V_{X4}$$

$$V_{XT} = 4 - 6 - 21 - 5 = \underline{\underline{-28 V}}$$

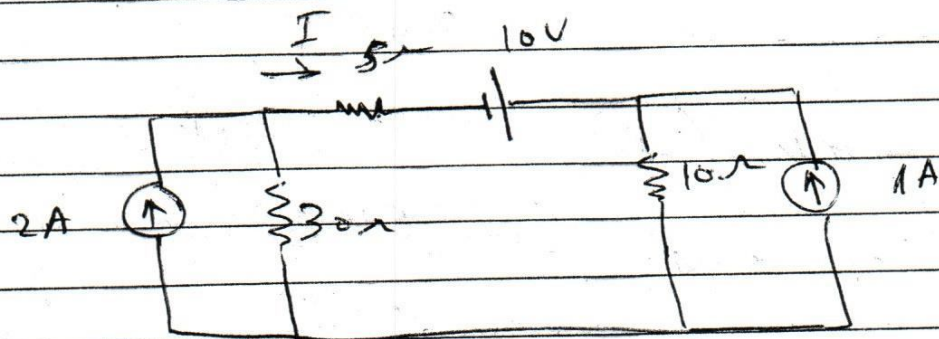
Exp. Find I for the circuit shown below by using superposition theorem;



1- effect 2A:

$$I' = 2 \times \frac{30}{45}$$


$$= \underline{\underline{1.333 A}}$$

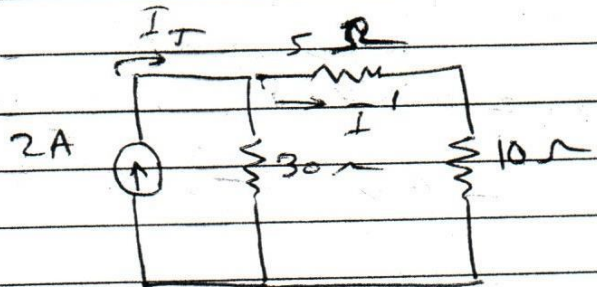

2- effect 1A:


$$I'' = 1 \times \frac{10}{45}$$

$$= \underline{\underline{0.222 A}}$$

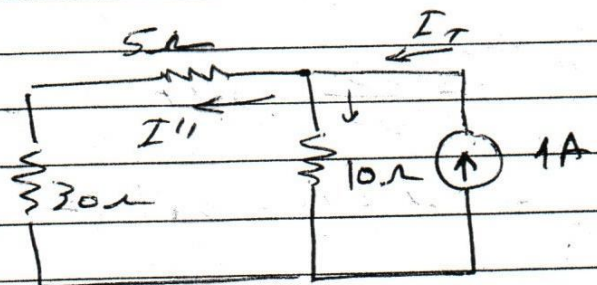

3- effect 10V:
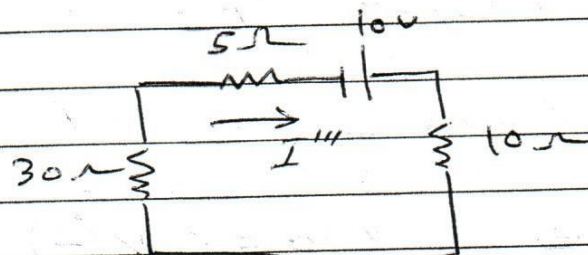
$$I''' = \frac{10}{45} = \underline{\underline{0.222 A}}$$



$$I = 1.333 - 0.222 + 0.222 = \underline{\underline{1.333 \text{ A}}}$$

Exp.


For the circuit, find current I , by using superposition theorem?

1- effect 3A:

$$20 \parallel 30 = 12 \Omega$$

$$12 \Omega + 20 = 32 \Omega$$
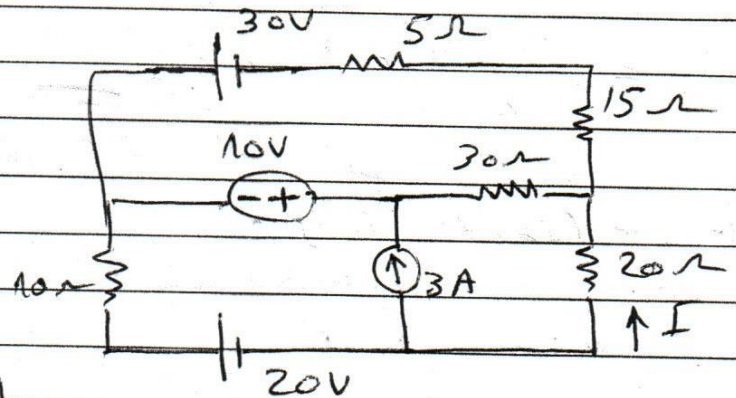
$$I' = 3 \times \frac{10}{42} = 0.714 \text{ A}$$




2- effect 30V:

$$30 \parallel 30 = 15 \Omega$$


$$15 + 15 + 5 = 35 \Omega$$
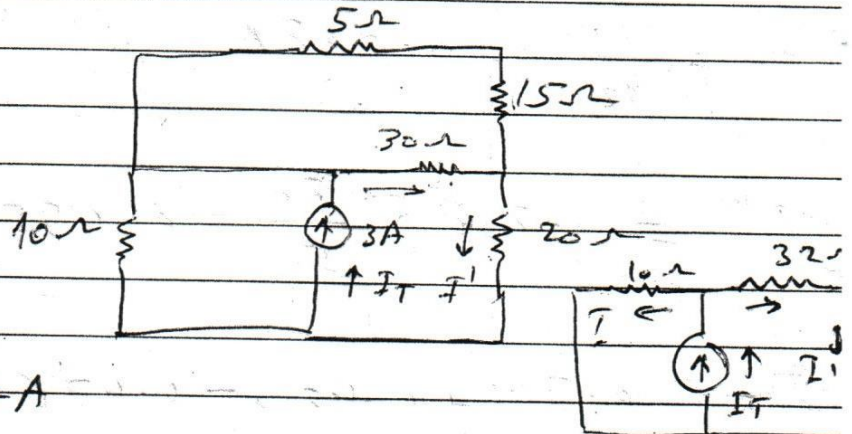
$$I_T = \frac{30}{35} = 0.857 \text{ A}$$



$$I'' = 0.857 \times \frac{30}{60}$$

$$= 0.428 \text{ A}$$

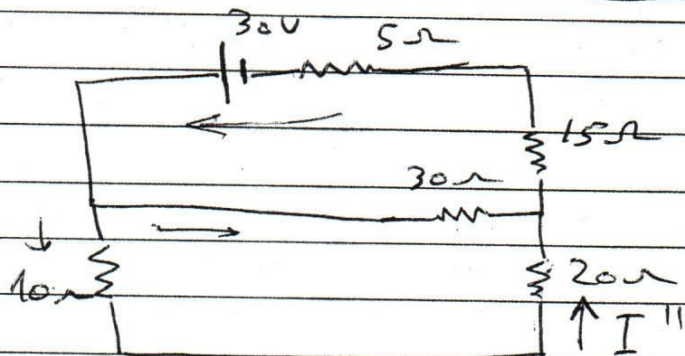


21

3 - effect 20V :

$$20 \parallel 30 = 12 \Omega$$

$$R_{eq} = 30 + 12 = 42 \Omega$$
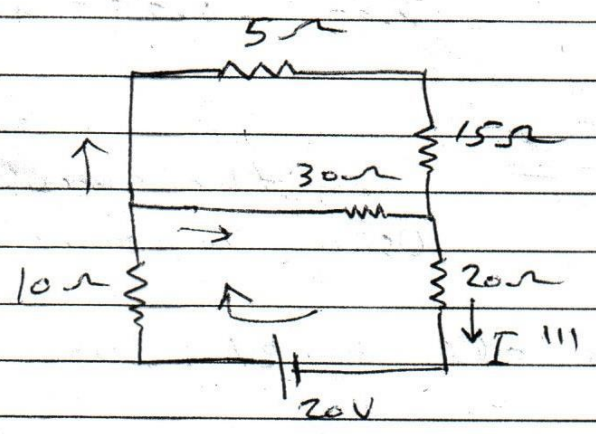
$$I_T = \frac{20}{42} = 0.476 A = \underline{\underline{I^{III}}}$$




4 - effect 10V :

$$30 \parallel 20 = 12 \Omega$$

$$12 + 30 = 42 \Omega$$

$$I_T = \frac{10}{42} = 0.238 A$$

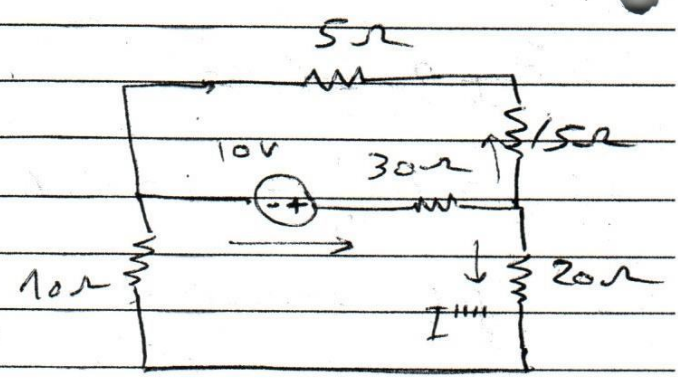


$$I^{''''} = 0.238 \times \frac{20}{50} = 0.095 A$$

$$I = -0.714 + 0.428 - 0.476 - 0.095 = \underline{\underline{-0.856 A}}$$

The Thevenin Theorem

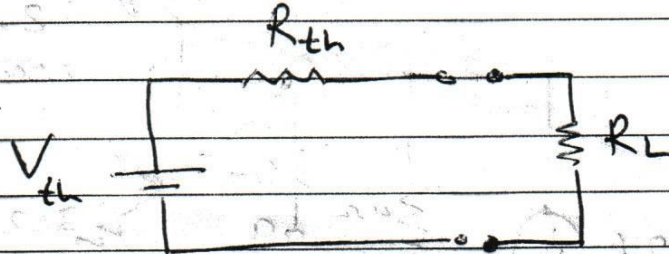The TT can transform any electric circuit to equivalent circuit (Thevenin):



This Theorem used when the circuit have voltage sources with resistances only.

Solution steps:

take the device who must to calculate his thevenin circuit for him and put in his place A, B. Calculate the equivalent resistance between A, B and this value equal $R_{eq} = R_{th} = R_N$ and calculate the voltage

between A, B, this value equal V_{th} and in the finished drawing the equivalent circuit.


- 1- take the device and put A, B.
- 2- Calculate the voltage between A, B (V_{th}).
- 3- put short circuit between A, B and calculate the current ($I_{s.c}$) $I_{s.c} = I_N$.
- 4- we can to calculate the resistance $R_{th} =$

$$R_N = R_{th} = \frac{V_{th}}{I_{s.c}}$$

$$I_{s.c} = \frac{V_{th}}{R_{th} + R_L}$$

Exp.

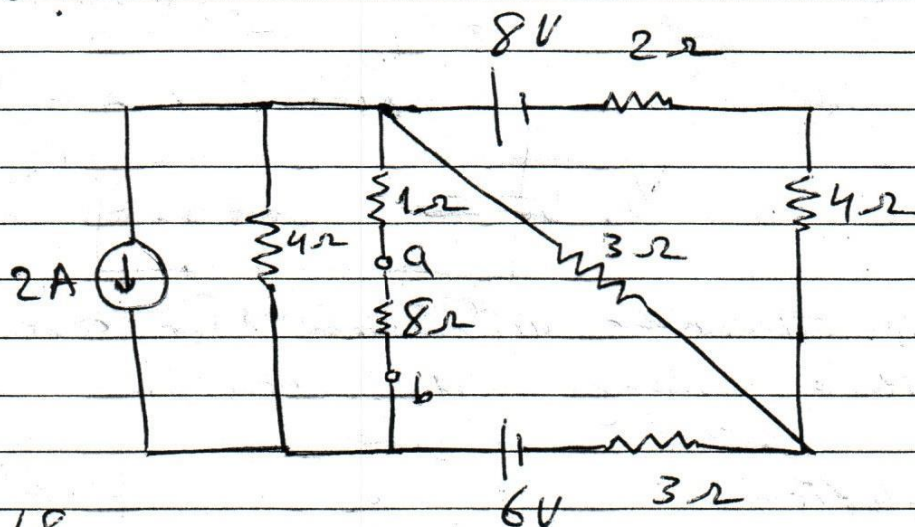Find the power dissipated in 8Ω using theorem?



$$6 \parallel 3 = \frac{18}{9} = 2\Omega$$

$$2 + 3 = 5\Omega$$


$$5 \parallel 4 = \frac{20}{9} = 2.222\Omega$$

$$2.222 + 1 = 3.222\Omega$$

$$R_{th} = 3.2\Omega$$

$$V_{th} = V_{ab} = V_{4\Omega}$$

$$V_{4\Omega} = I \times R$$

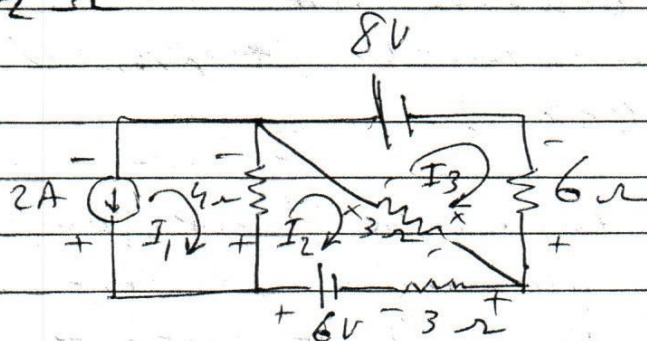

By using mesh analysis:

AT loop ① KVL:

$$I_1 = -2A$$

At Loop (2) KVL:

$$6 - 3I_2 - 4(I_2 - I_1) - 3(I_2 - I_3) = 0$$

$$6 - 3I_2 - 4I_2 + 4I_1 - 3I_2 + 3I_3 = 0$$

$$6 - 6I_2 - 4I_2 + 3I_3 - 8 = 0$$

$$-10I_2 + 3I_3 = 2 \quad (1)$$

At Loop (3) KVL:

$$-8 + 6I_3 - 3(I_3 - I_2) = 0$$

$$-8 + 6I_3 - 3I_3 + 3I_2 = 0$$

$$3I_2 + 3I_3 = 8 \quad (2)$$

By subtracting (1) and (2)

$$-10I_2 + 3I_3 = 2$$

$$+3I_2 + 3I_3 = 8$$

$$-13I_2 = -6 \Rightarrow I_2 = \frac{-13}{-6} = 2.16 \text{ A}$$

From eq. (1) we can find I_3 :

$$-10 \times 2.16 + 3I_3 = 2$$

$$-21.6 + 3I_3 = 2 + 21.6 = 23.6$$

$$I_3 = \frac{23.6}{3} = 7.86 \text{ A}$$

$$V_{4\Omega} = 4 \times (I_2 - I_1) = 4 \times (2.16 + 2) = 4 \times 4.16 = 16.64$$



$$V_{th} = 16.64 \text{ V}$$


$$I = \frac{V_{th}}{R_{th} + 8} = \frac{16.64}{3.2 + 8} = \frac{16.64}{11.2} = \underline{\underline{1.485 \text{ A}}}$$

$$P_R = I^2 \times R = (1.485)^2 \times 8 = 2.205 \times 8$$


$$P_R = 17.6418 \text{ W}$$

Exp.

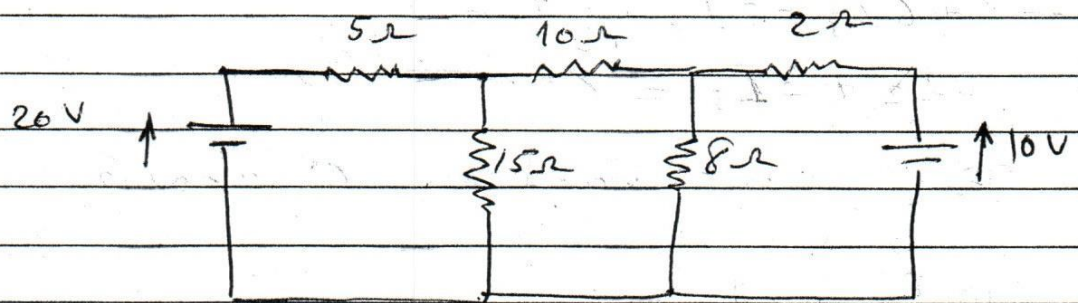Calculate the current in the resistance 10Ω by using thevenin theorem for the following circuit?



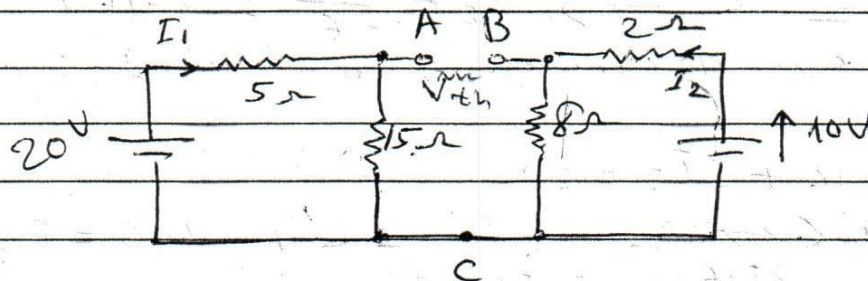When we open the branch ~~where~~ ~~which~~ ~~his~~ resistor 10Ω the circuit will be:




$$I_1 = \frac{20}{5 + 15} = 1 \text{ A} \Rightarrow V_{AC} = 1 \times 15 = 15 \text{ V}$$

$$I_2 = \frac{10}{2 + 8} = 1 \text{ A} \Rightarrow V_{BC} = 1 \times 8 = 8 \text{ V}$$

$$\therefore V_{AB} = V_{AC} - V_{BC} = 15 - 8 = 7V = V_{th}$$

$$R_{eq} = \frac{5 \times 15}{5 + 15} + \frac{8 \times 2}{8 + 2} = 3.75 + 1.6 = 5.35 \Omega = R_{AB}$$

$$= R_{th}$$

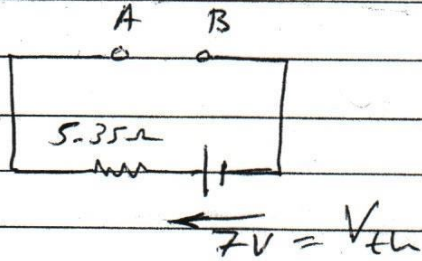

$$R_{eq} = R_{th} + 10 = 5.35 + 10 = 15.35 \Omega$$


$$I_{th} = \frac{V_{th}}{R_{th} + 10} = \frac{7}{15.35} = 0.46A$$


Norton's Theorem

this theorem is same as a Thevenin's but here we ~~not~~ use the current source ~~we place~~

Exp

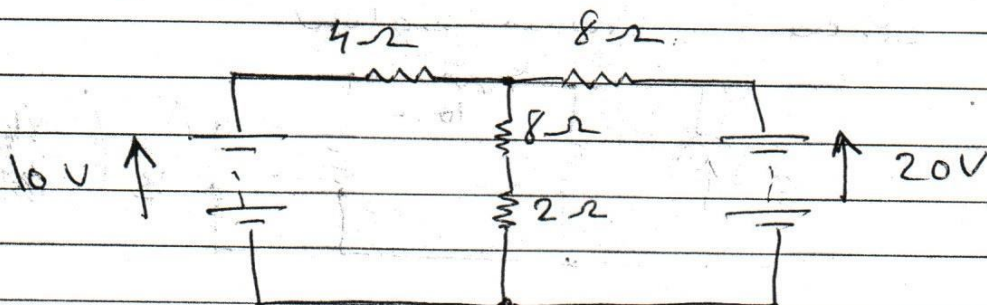calculate the voltage drop across the resistance (2Ω) of the following circuit by using Norton theorem?



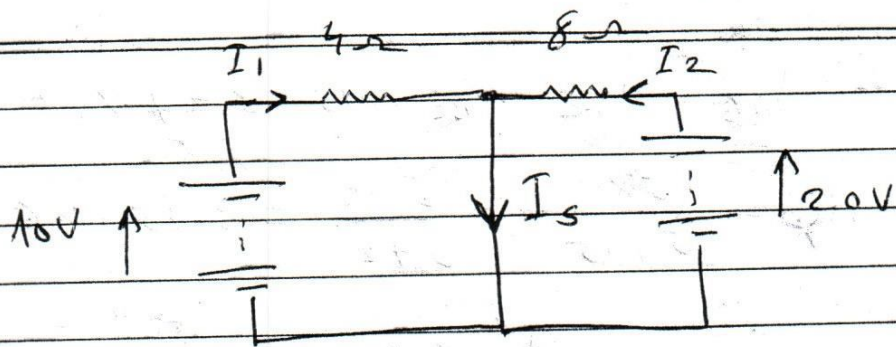


$$I_1 = \frac{10}{4} = 2.5 \text{ A}$$

$$I_2 = \frac{20}{8} = 2.5 \text{ A}$$

$$I_s = I_1 + I_2 = 5 \text{ A}$$
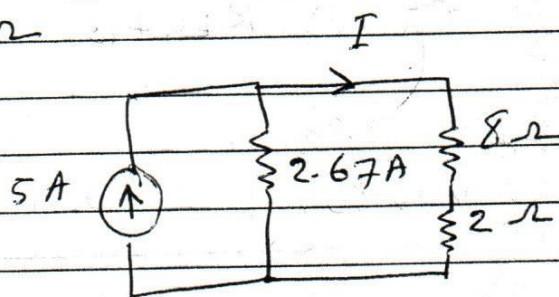
$$R_N = \frac{4 \times 8}{4 + 8} = 2.67 \text{ A}\Omega$$




$$I = \frac{2.67}{2.67 + 10} \times 5 = 1.06 \text{ A}$$

$$V = 1.06 \times 2 = \underline{\underline{2.12 \text{ V}}}$$

Exp.

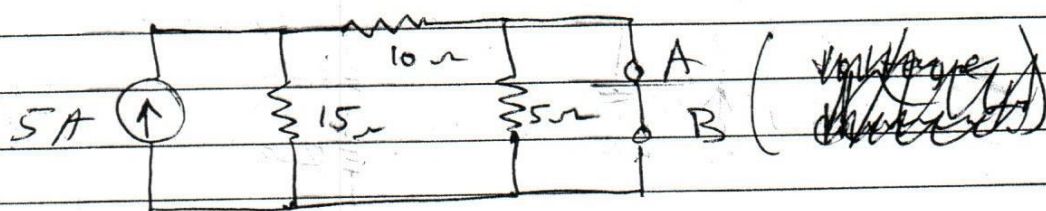Find Norton equivalent circuit for the circuit shown below





40


$$R_N = \frac{25 \times 5}{30} = 4.166 \Omega$$

$$R_N = \frac{15 \times 5}{25 + 5} = 4.166 \Omega \quad (\text{circuit diagram})$$

$$I_N = 5 \times \frac{15}{15 + 10} = 3 \text{ A}$$

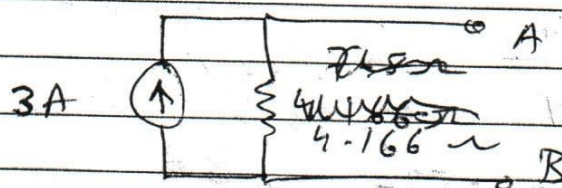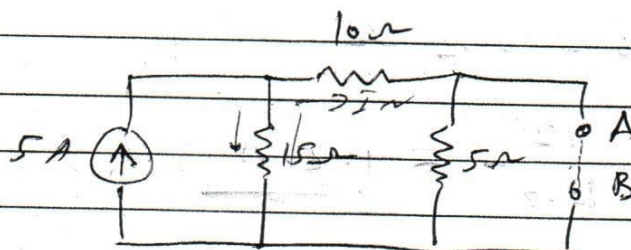
EX.

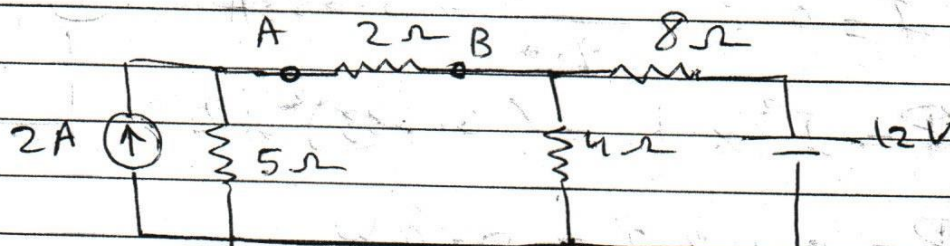Calculate the power dissipated in (2Ω) using Norton's theorem?



$$R_{th} = R_N = R_{eq}$$

$$8 // 4 = \frac{32}{12} = 2.66 \Omega$$

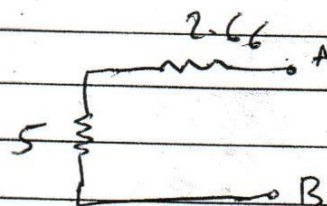


$$2.66 + 5 = 7.6 \Omega$$

By using superposition theorem

① effect $2\text{A} \Rightarrow$
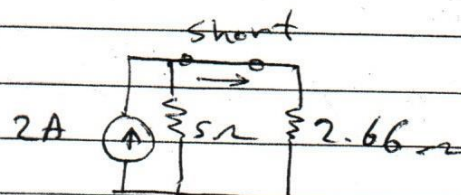
$$I_1 = 2 \times \frac{5}{7.6} = 1.315 \text{ A}$$




$$P = 0.4 \times 2 = 0.8 \text{ W}$$

$$P = I^2 \times R = (0.633)^2 \times 2$$

$$I = 0.8 \times \frac{7.6}{9.6} = 0.633 \text{ A}$$

$$I_N = 0.8 \text{ A}$$

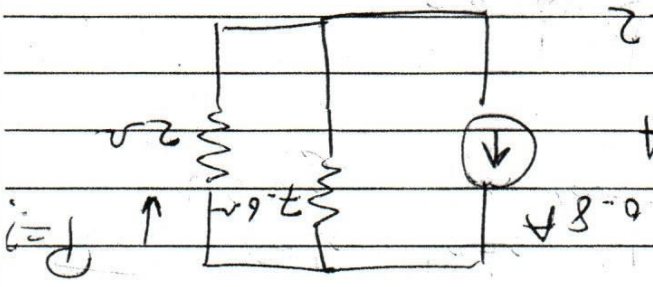

$$I_{S.C} = 1.315 - 0.522 = 0.8 \text{ A}$$


$$I_2 = 1.2 \times \frac{9}{4} = 0.522 \text{ A}$$

$$I_1 = \frac{1.2}{10.2} = 1.2 \text{ A}$$

$$2.2 + 8 = 10.2 \Omega = R_{eq}$$

$$5.114 = \frac{20}{9} = 2.22$$

② effect 12V

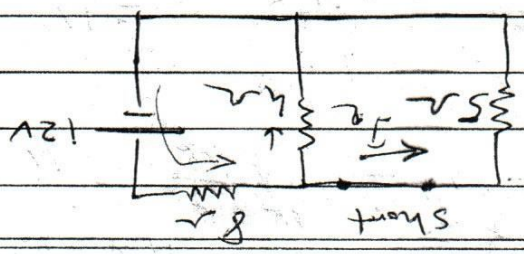

44


EXP

Find maximum Power in R ?
by using thevenin's theorem.

AT maximum power

$$R_L = R_{th} = R_N$$

$$R_{th} = ?$$

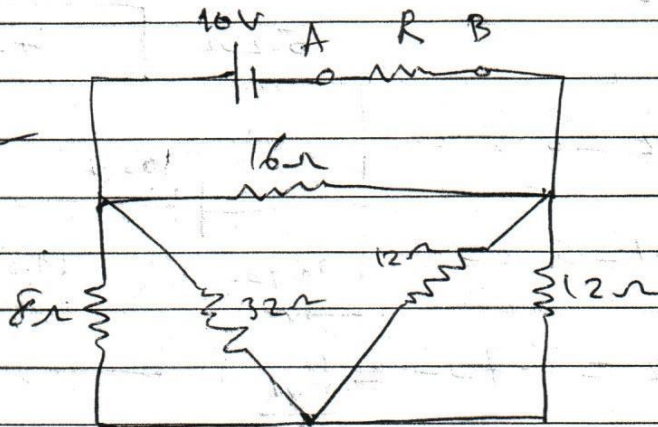


$$12 \parallel 12 = 6 \Omega$$

$$8 \parallel 32 = 6.4 \Omega$$

$$6 + 6.4 = 12.4 \Omega$$

$$12.4 \parallel 16 = 7 \Omega$$

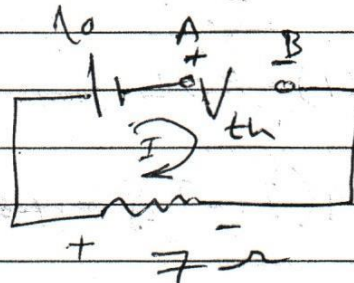

$$R_{th} = 7 \Omega$$


$$7I - 10 - V_{th} = 0 \quad (I=0 \text{ open circuit})$$

$$V_{th} = -10 \text{ V}$$

$$P_{max} = \frac{(V_{th})^2}{4R_{th}} = \frac{(-10)^2}{4 \times 7} = \frac{100}{28} = 3.6 \text{ WATT}$$

Exp.

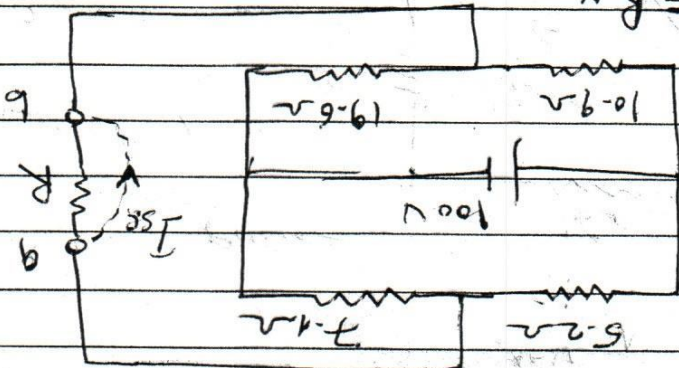Find the maximum power transfer in R_L using Norton theorem?



$$10.9/5.2 = 3.52$$

$$19.6/17.1 = 5.22$$

$$3.52 + 5.2 = 8.72 = R_N$$

$$I_T = \frac{100}{8.7} = 11.5A$$

$$I_{5.2} = I_3 - I_2$$

AT loop (1) KVL:

$$100 - 10.9(I_1 - I_2) - 19.6(I_1 - I_3) = 0$$

$$30.5I_1 - 10.9I_2 - 19.6I_3 = 100 \quad \text{--- (1)}$$

AT loop (2) KVL:

$$-5.2I_2 - 10.9(I_2 - I_1) = 0$$

$$10.9I_1 - 16.1I_2 = 0 \quad \text{--- (2)}$$

AT loop (3) KVL:

$$-7.1I_3 - 19.6(I_3 - I_1) = 0$$

$$19.6I_1 - 26.7I_3 = 0 \quad \text{--- (3)}$$

(42)

By adding ~~(2)~~ and (3) :

$$10.9 I_1 - 16.1 I_2 = 0 \quad (2)$$

$$19.6 I_1 - 26.7 I_3 = 0 \quad (3) \quad * 7.1$$

+

$$30.5 I_1 - 16.1 I_2 - 26.7 I_3 = 0 \quad (4)$$

by ~~subtracting~~ (2)

by subtracting (1) and (4)

$$30.5 I_1 - 10.9 I_2 - 19.6 I_3 = 100 \quad (1)$$

$$-30.5 I_1 + 16.1 I_2 + 26.7 I_3 = 0 \quad (4)$$

Sub.

$$5.2 I_2 + 7.1 I_3 = 100 \quad (5) \quad * 26.7$$

By add. (3) and (5)

$$138.84 I_2 + 189.57 I_3 = 2670 \quad (5)$$

$$139.16 I_1 - 189.57 I_3 = 0 \quad (3)$$

+

$$139.16 I_1 + 138.84 I_2 = 2670 \quad (6) \quad * 16.1$$

by add. (2) and (6) we get:

$$2240.476 I_1 + 2235.324 I_2 = 4298.7 \quad (6)$$

$$-1513.356 I_1 - 2235.324 I_2 = 0 \quad (2)$$

$$3753.832 I_1 = 4298.7$$

$$I_1 = \frac{42987}{3753.832} = 11.45 \text{ A}$$

By substitution in (2)

$$10.9 \times 11.45 - 16.1 I_2 = 0$$

$$124.82 = 16.1 I_2 \Rightarrow I_2 = \frac{124.82}{16.1} = 7.75 \text{ A}$$

\Rightarrow from eq. (1)

$$30.5 \times 11.45 - 10.9 \times 7.75 - 19.6 I_3 = 100$$

$$349.225 - 84.475 - 19.6 I_3 = 100$$

$$264.75 - 100 = 19.6 I_3$$

$$I_3 = \frac{164.75}{19.6} = 8.405 \text{ A}$$


$$I_{s.c} = I_3 - I_1 = 8.405 - 11.45 = -3.044 \text{ A}$$

$R_L = R_N = R_{th}$ at max. power

$$V_{th} = I_N \times R_N = -3.044 \times 8.7 = -26.48 \text{ V}$$

$$P_{max} = \frac{(V_{th})^2}{4 R_{th}} = \frac{701.338}{4 \times 8.7}$$


$$= 20.153 \text{ Watt}$$

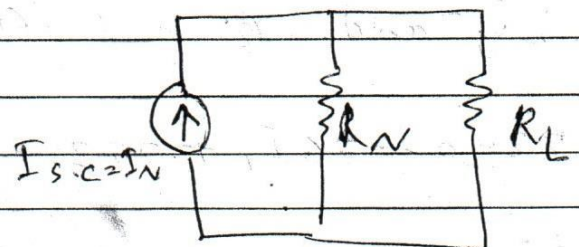


Generation of alternating current, Sinusoidal Current

Alternating current (AC): it is a current ~~who~~ which have a variable value and ~~var~~ relatively with time.

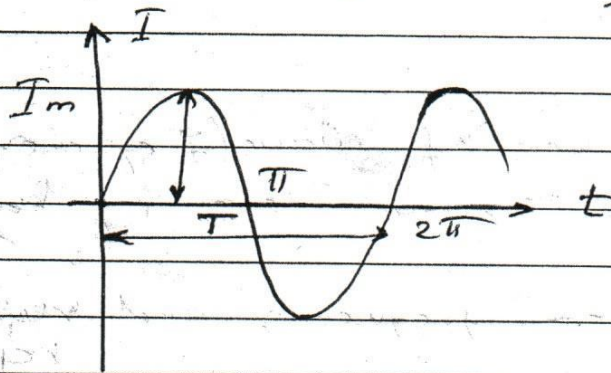
The AC current can act as a wave. The wave can be ~~sinusoidal~~ ^{sin} wave, square, sawtooth and triangle as the following




Sin wave

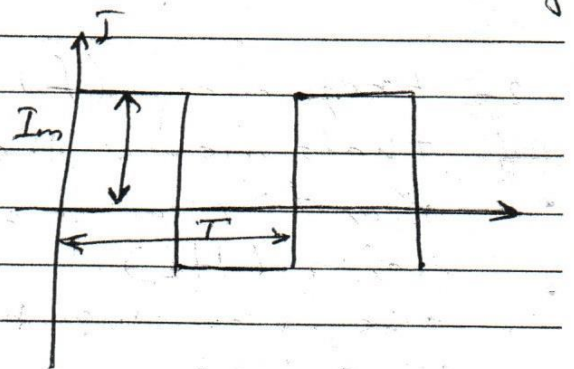

Square wave

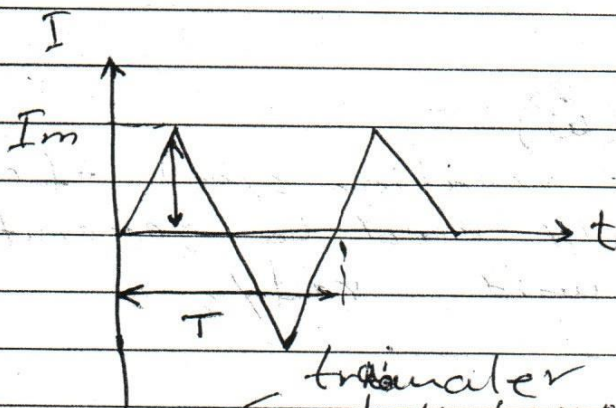

Triangular wave

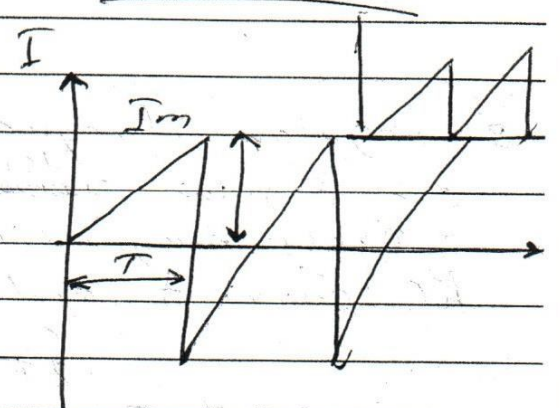


Sawtooth wave

The wave may be current, voltage and Power.

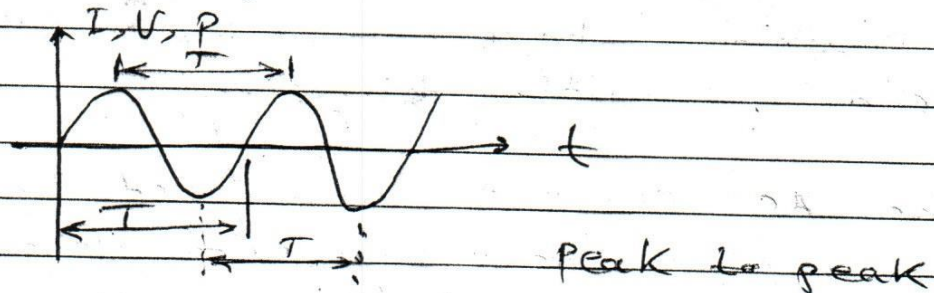1. Period time (T)

The time which is very important for finishing complete one wave cycle of wave and measured by second (s)



2. Frequency (f)

That means the number of wave (frequency) repeating in time unit, and measured by Hertz (Hz).

The relationship between frequency and repeating time is:

$$f = \frac{1}{T} \text{ — Hz } \left(\frac{1}{s} \text{ or } s^{-1} \right)$$


3. Angular frequency (ω)

or Angular ^{Velocity} ~~speed~~ its rotation speed of coil a cross magnetic field used to generate AC current and its unit rad/s :

$$\omega = 2\pi f = \frac{2\pi}{T}$$


4 phase shift (ϕ), that's meaning is a value of signal moving from the original place as measured by (rad) or (degree).

how to measure the ϕ :

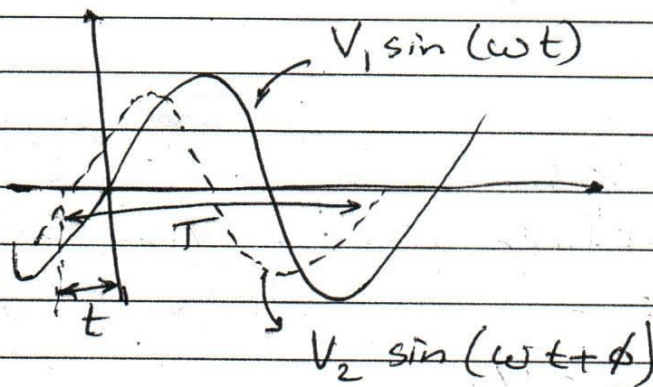


$$\phi = \frac{t}{T} \times 360^\circ$$

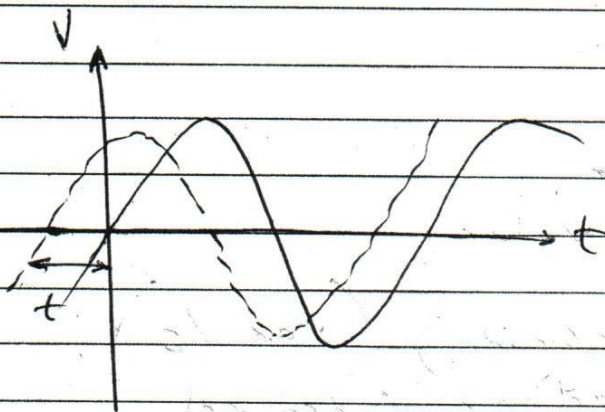if the signal is (Lead) over the original signal that's mean the phase shift must be positive but when the signal is (Lag) over the original signal, the phase shift must be negative.




Lead signal
(phase shift positive)

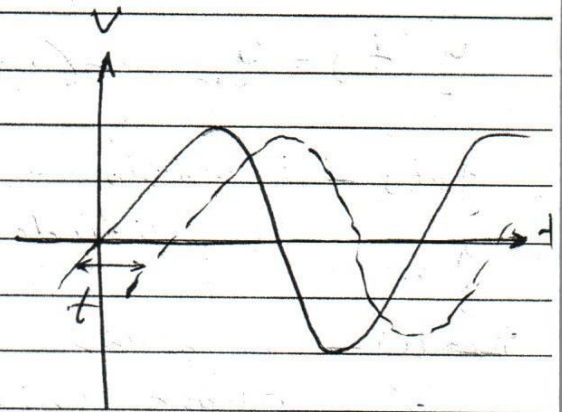

Lag signal
(phase shift negative)

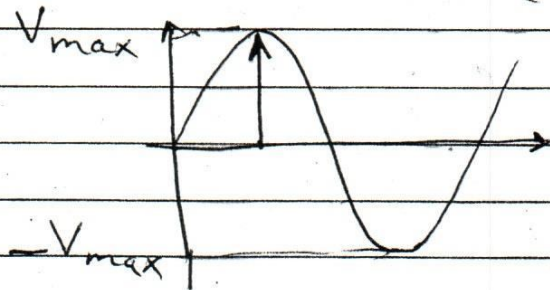5. Amplitude or maximum value:
that mean max peak which the wave can
state in the peak (V_p)



6. peak-to-peak value
that mean the amplitude measure from the
peak to peak:

$$V_{p-p} = 2V_p$$

7. Instantaneous Value,
the value of wave in the limiting time.

The general mathematic equation for the
sin wave is:

$$y(t) = y_m \sin(\omega t + \phi)$$

$y(t)$ - Instantaneous value

y_m - Amplitude (max value)

ω - angular speed (velocity) (rad/s)

ϕ - phase shift (rad) or ($^\circ$ degree)

Note: When calculating of Instantaneous value
must convert (ϕ) to unit rad:

$$\phi_{\text{rad}} = \phi^\circ \times \frac{\pi}{180^\circ}$$

Effective Value (root mean square Value)

dissipation power cause by AC current across resistance for limit time equal dissipation power cause by DC current across the same resistance for same time.

Give by math. relationship:

$$y_{rms} = \sqrt{\frac{1}{T} \int_0^T (y(t)^2) dt} \quad \left(V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V(t)^2) dt} \right)$$

For sine wave:

$$V(t) = V_p \sin(\omega t) \quad I(t) = I_m \sin \omega t$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2(\omega t) dt}$$

$$= V_p \sqrt{\frac{1}{T} \int_0^T \frac{1 - \cos(2\omega t)}{2} dt}$$

$$= V_p \sqrt{\frac{1}{2T} [T - 0]} = \frac{V_p}{\sqrt{2}} \quad V_{max}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

Average Value V_{av}

$$V_{av} = \frac{1}{T} \int_0^T V(t) dt$$

For sine wave (Voltage)

$$V_{av} = \frac{V_{max}}{\pi}$$

(current)

$$I_{av} = \frac{1}{T} \int_0^T i(t) dt \Rightarrow I_{av} = \frac{2 I_{max}}{\pi}$$

~~Adv of current~~

$$\left| \sin \theta = \cos \left(\theta - \frac{\pi}{2} \right) \quad \cos \theta = \sin \left(\theta + \frac{\pi}{2} \right) \right|$$

Form Factor (K_F)

That's mean relatively between the effective and average value:

$$(F.F) K_F = \frac{V_{rms}}{V_{av}}$$

Peak Factor (K_P) (K_{max})

$$K_P = \frac{V_{max}}{V_{rms}}$$